

Energy Harvesting ULP PMIC for Smart Sensor Node


Enerharv 2018 – Power Management

Séamus O'Driscoll, Tim Daly, James McCarthy, Gerry McGlinchey, Ivan O'Connell, Michael Hayes


28th May 2018





ICT4EE Systems
(Energy Efficiency)

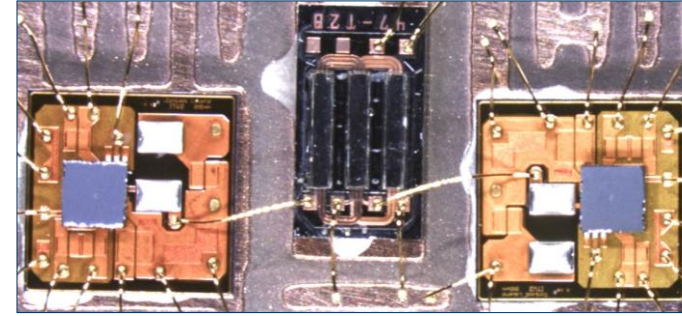

PWRSiP, PWRSoC

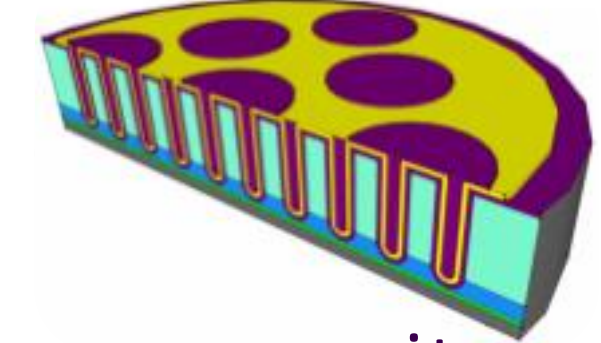


Solid State Supercapacitors

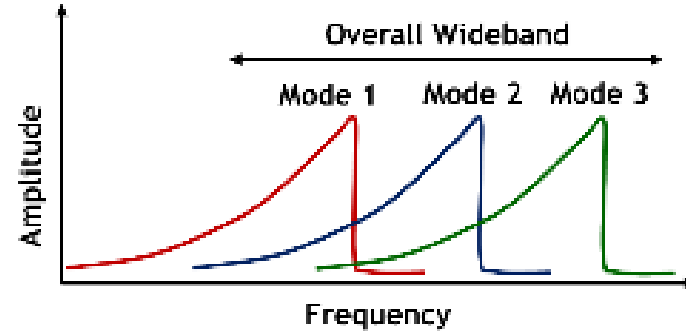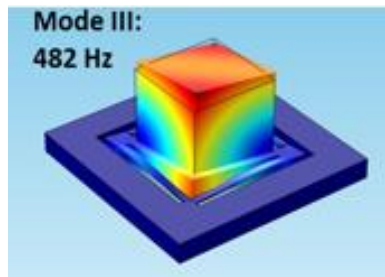


Vibrational Energy Harvester

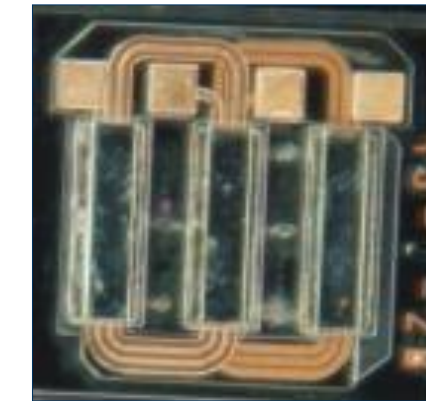Materials
Structures
Magnetics on Silicon





Solid State
Energy Cells

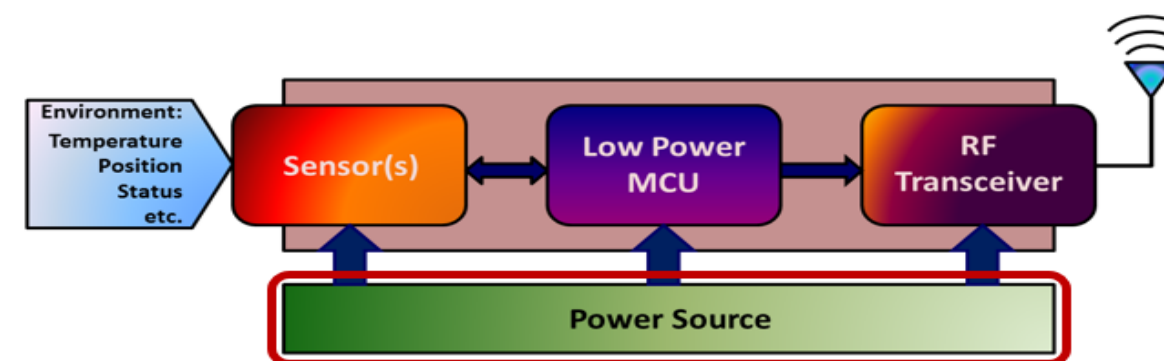

WSN

Material Model & Synthesis

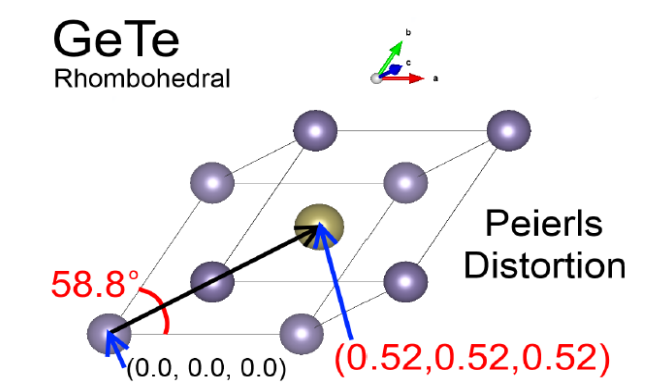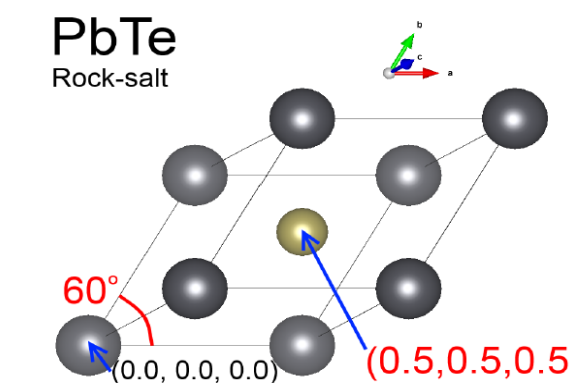Mix materials with slightly different atomic arrangements:



Integrated Power Systems and PMICs

Integrated Systems Design

Power Conversion & PMIC at Tyndall:





EnerHarv 2018



Smart Sensor Power
Ambient Energy Harvesting
Implantable Power
Couplers, EMT

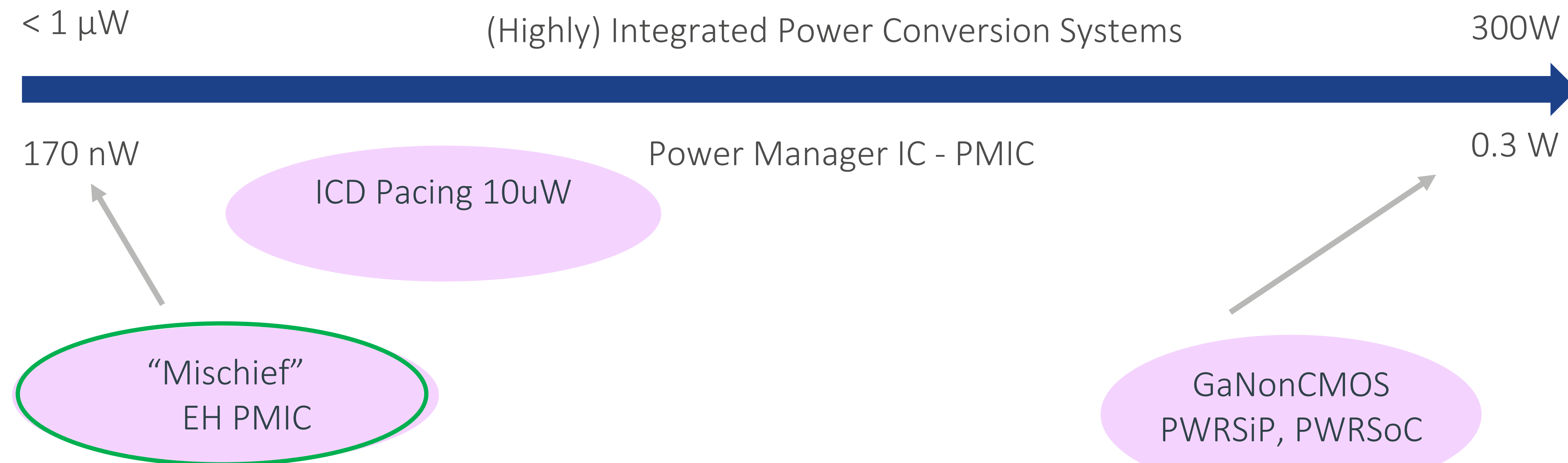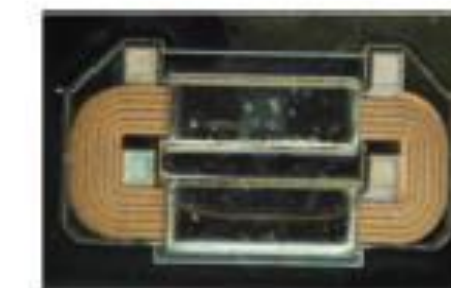DC-DC: POL, VR, SoC
Switch Mode Inductor or Hybrid Topology
Advanced Magnetic Component Designs 1-100MHz
BEOL Wafer Scale RDL based Thin Film Magnetic Materials,
Substrate Embeddable



Ultra Low Power (ULP) PMICs

Low Bandwidth and Low Average Data “*battery-less*” (maintenance-free) systems

Or

Battery Life extension to 25+ years

Power and Energy Data points

Short-range (BLE) Wireless SoC
Wearables - $1\mu\text{A}$ Idle with 32kHz & RTC
 $\sim 2.4\mu\text{W}$ average for radio for heart rate profile –
4bytes/s for 1h/day


Ocular (retina) implant system @ $\text{IDD}=50\text{nA}$

Hearing Aid DSP - $<100\mu\text{A}/\text{MIPs}$

SOA Technology Solid State Storage on
1.5mm X 1.5mm die will provide $\sim 15\mu\text{W.h}$
($10\mu\text{m}$ layer)

ICD Pacing Circuits 1-10uW

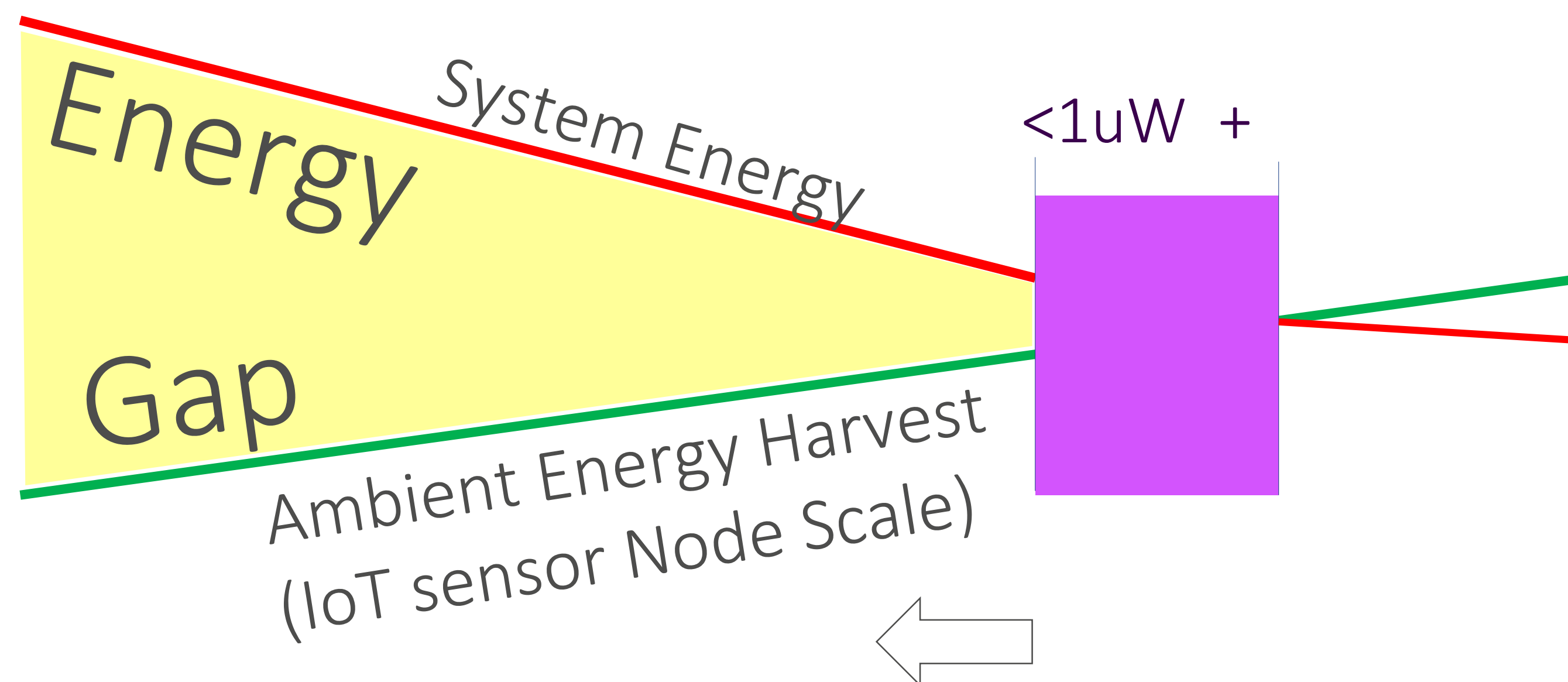ADuCM4050 Signal Processor $40\mu\text{A}/\text{MHz}$ active &
 680nA hibernate




Wide Dynamic Range & Heavily Duty Cycled Loads and Sources



Solar cells

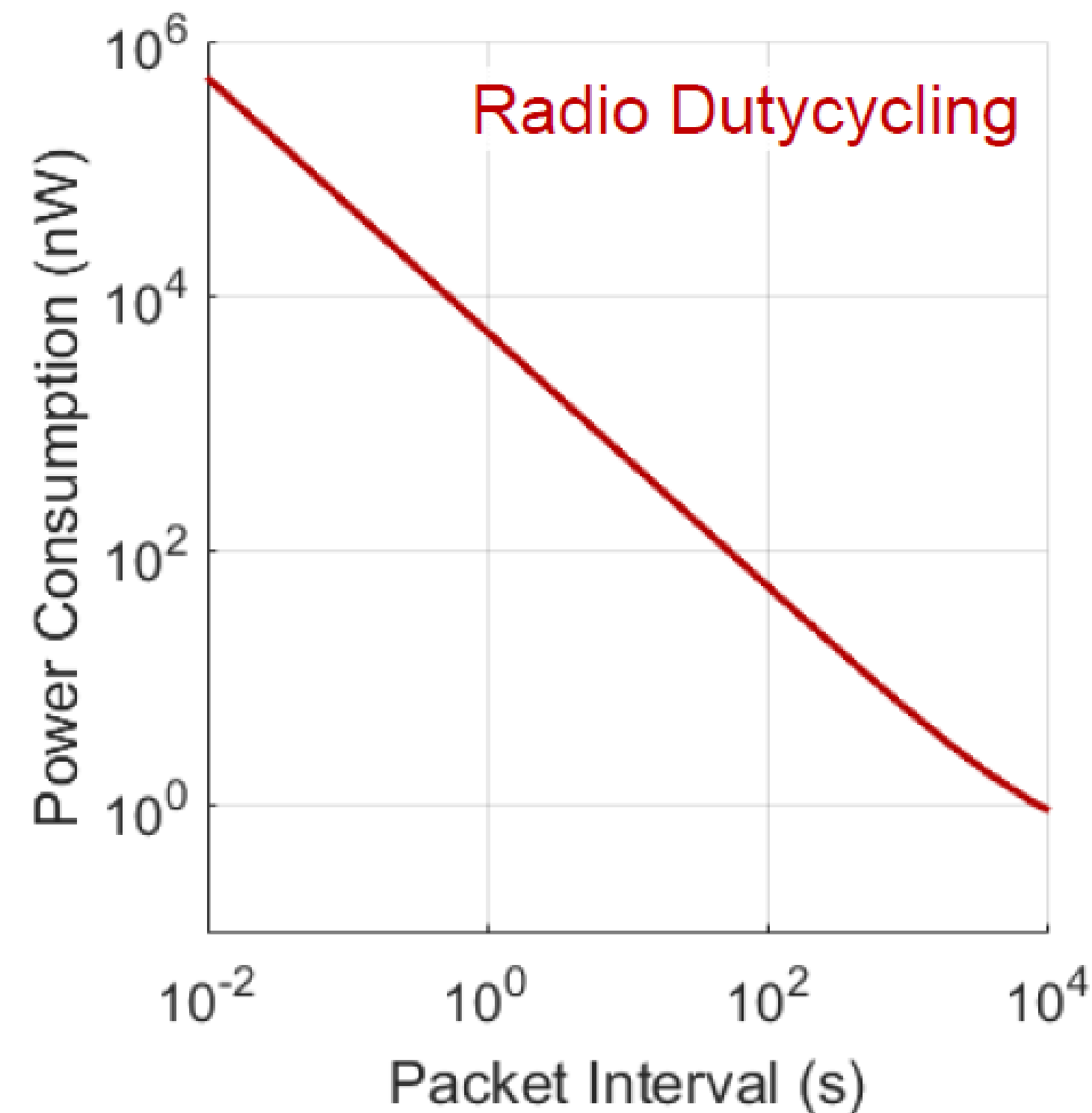- 100klux outdoors
 - 10lux indoors
 - Upto 10^4 dynamic range of available power
 - sub-nA with low area cells
- We measure 10 lux under a bench, 300 lux in “brightly lit” room
 - Solar Cell Dynamic Range 1×10^4 [Paidimarri et al, ISSCC '17]
 - Radio has 7.6×10^7 Dynamic Range [Paidimarri et al, ISSCC '15]



Control Silicon - ULP Wireless System Node

PMIC

Harvested Energy Conversion
Energy Storage Management
Battery Management
Regulated Voltages for the System

System Controller
Sensor Interface

Radio
RF

- The PMIC is currently generally a discrete IC
- But at ULP level the smart sensor node ***ideally requires a very high level of integration***


PMIC Voltages, Silicon Requirements and Control are very compatible with radio

Mixed-signal sensor interface circuits are very similar to those for energy source interaction and power control

Outer loop (tertiary) power control should ideally share resources with the system (host) controller.

- Accordingly “Mischief” represents flexible, mixed-signal, ULP-PMIC *platform IP offering*


Switch Mode Inductor Topologies

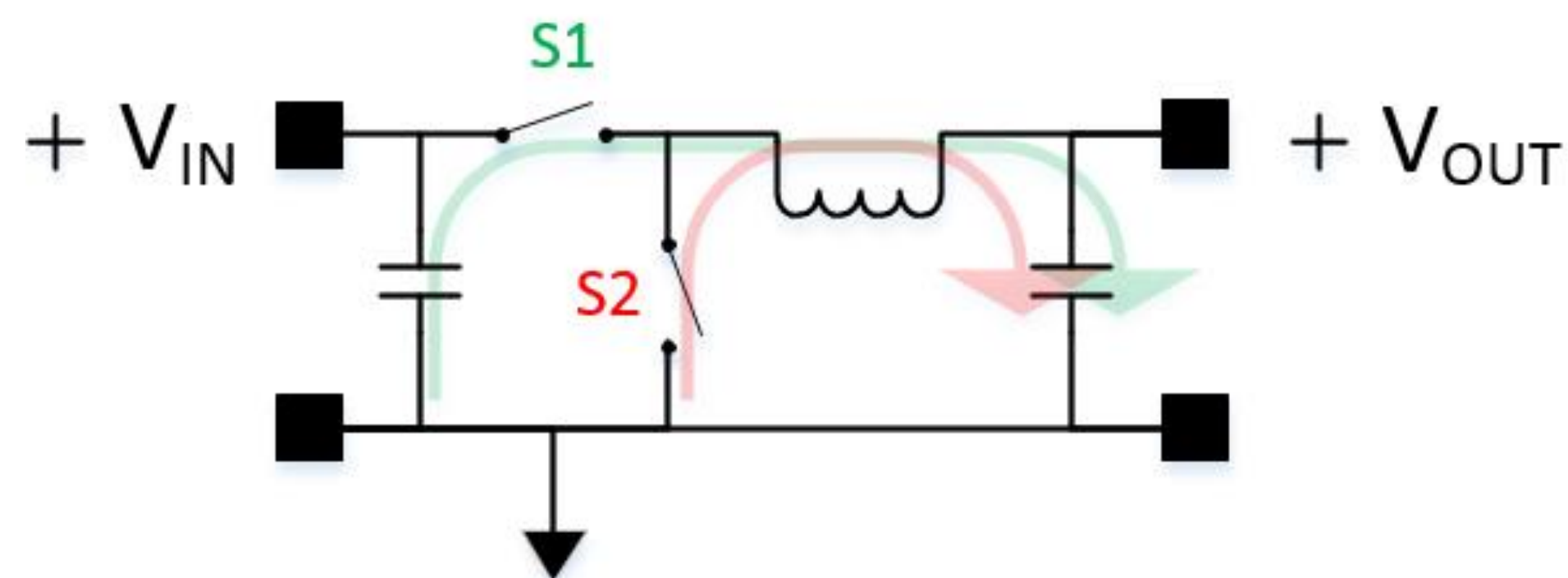

Buck
 $V_{IN} > V_{OUT}$


Inductors are beautifully
voltage compliant

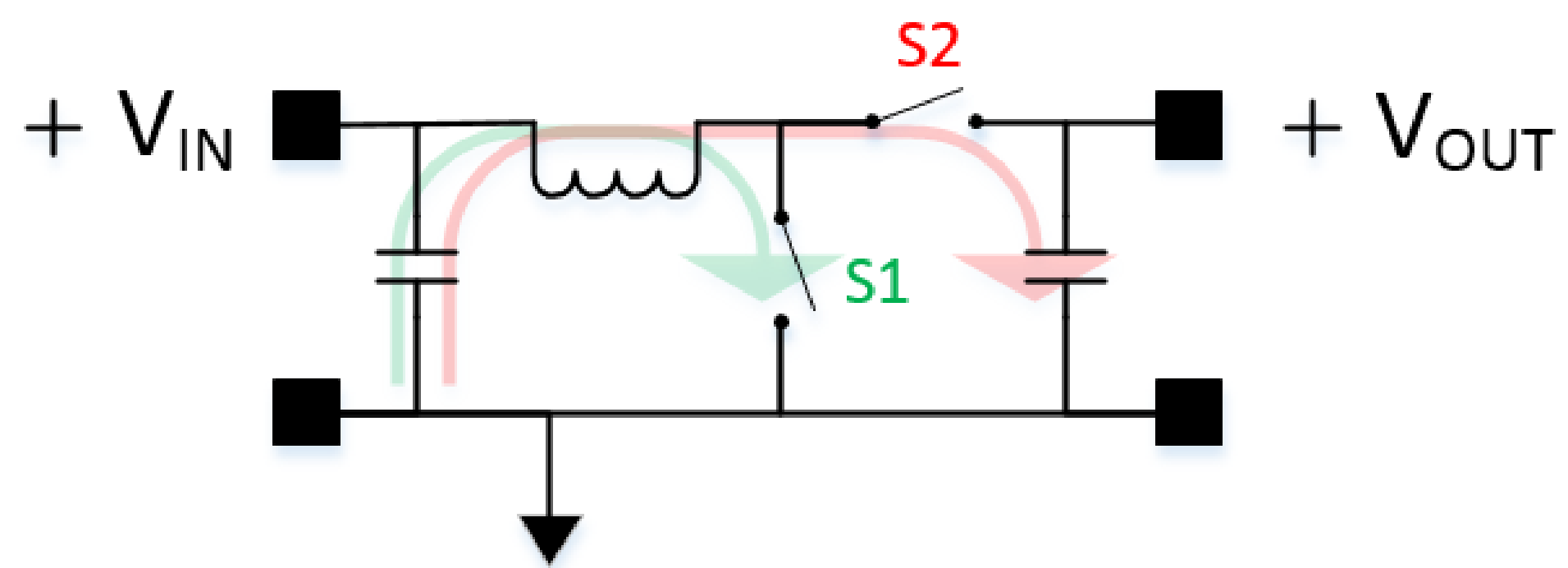Buck or Boost are more
efficient than Buck-Boost



Boost
 $V_{OUT} > V_{IN}$

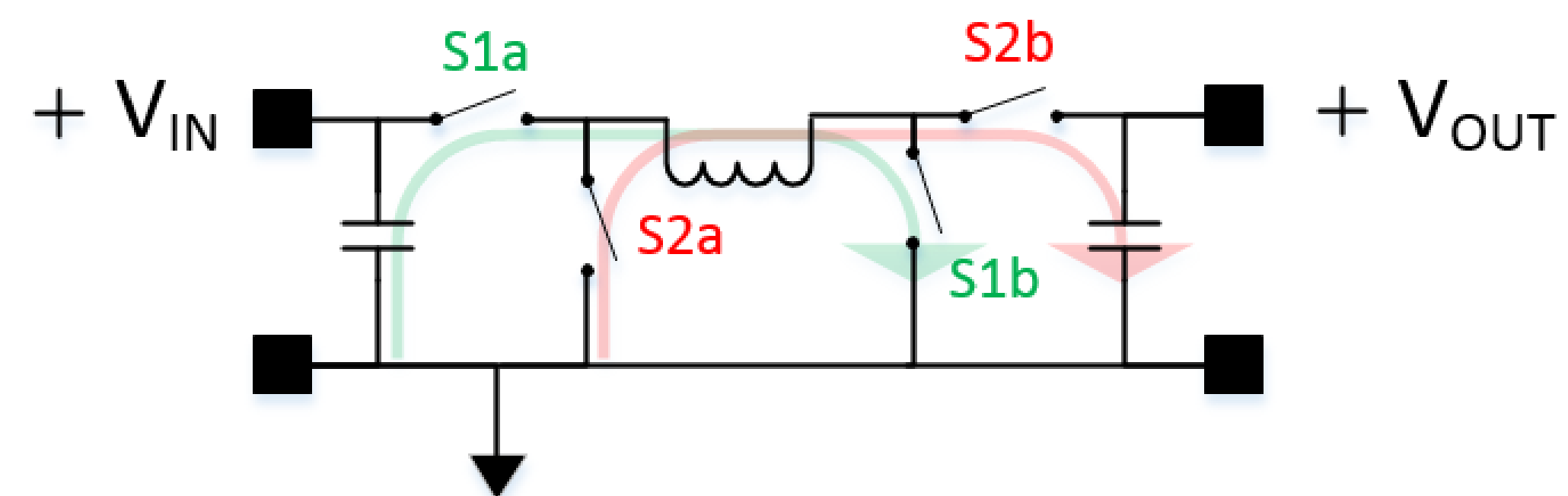Inductors are large when
looking for small Δi



Buck-Boost
 $V_{OUT} <, > V_{IN}$

PMIC Platform IP Development Goals

- Extend to sub - 1 μ W for emerging MICRO, MESO and MESO
 - Emerging Smart Sensor Node Controllers such as ADuCM4050 (40 μ A/MHz active, 680nA in hibernate mode, rapid start)
- Control flexibility to maximise energy transduction, energy storage and full-system energy efficiency
 - for a variety of energy harvester types: PV, TEG, Piezo, Electromagnetic and Electret
- Bring advanced intelligent control to the space (digital and mixed-signal)
- Leverage the benefits of digital assisting analog for low quiescent current PMIC circuits and references
- Create flexible solution IP to address power management challenge for IoT devices
- Cater for multiple system voltages, multiple input-output ratios and extend input voltage range
- A lot of niche smart sensor applications will require dynamic and intelligent fit with:
 - the application environment
 - the sensor
 - the radio
 - the energy source nature, type, MPPT, impedance
 - the storage




Enabling High Value, Novel, Next Generation Features

Digitised outer loop power/current set points for MPPT will enable features such as **performance monitoring of source and storage**


Charge profile tuning to suit **emerging battery chemistries**

VEH is AC and will be by Active Rectifier & DC-DC or Power Factor Improvement or Hybrid

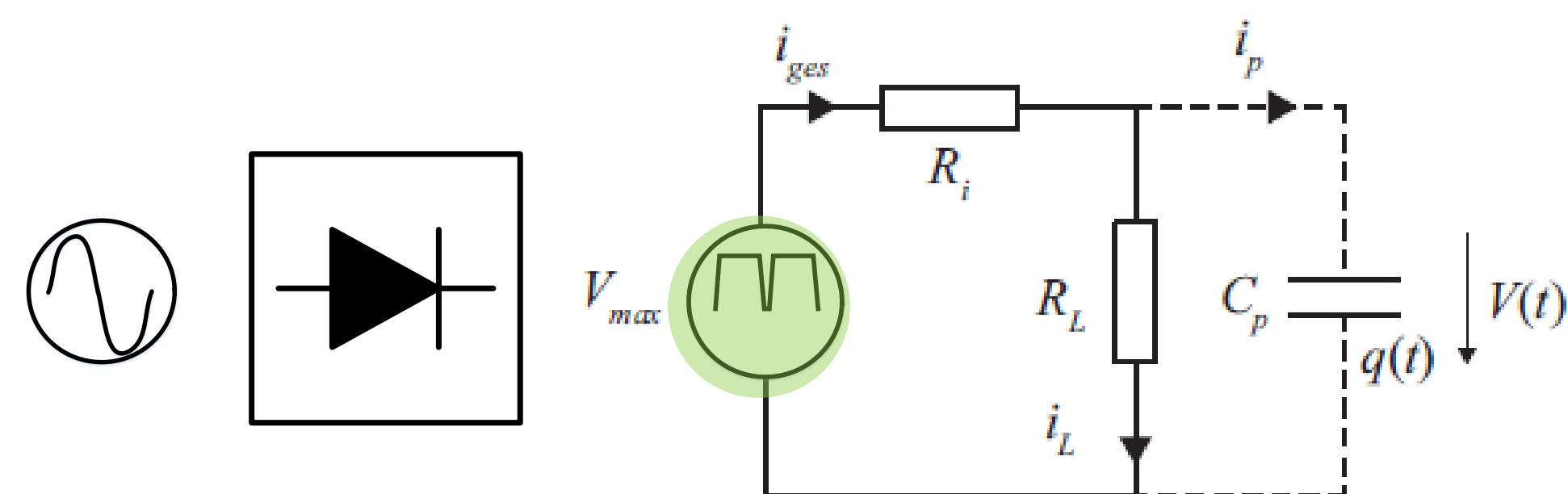Piezoelectric, electret devices tend to be current source in nature
Electromagnetic transduction tend to be voltage source in nature






Active Rectifier

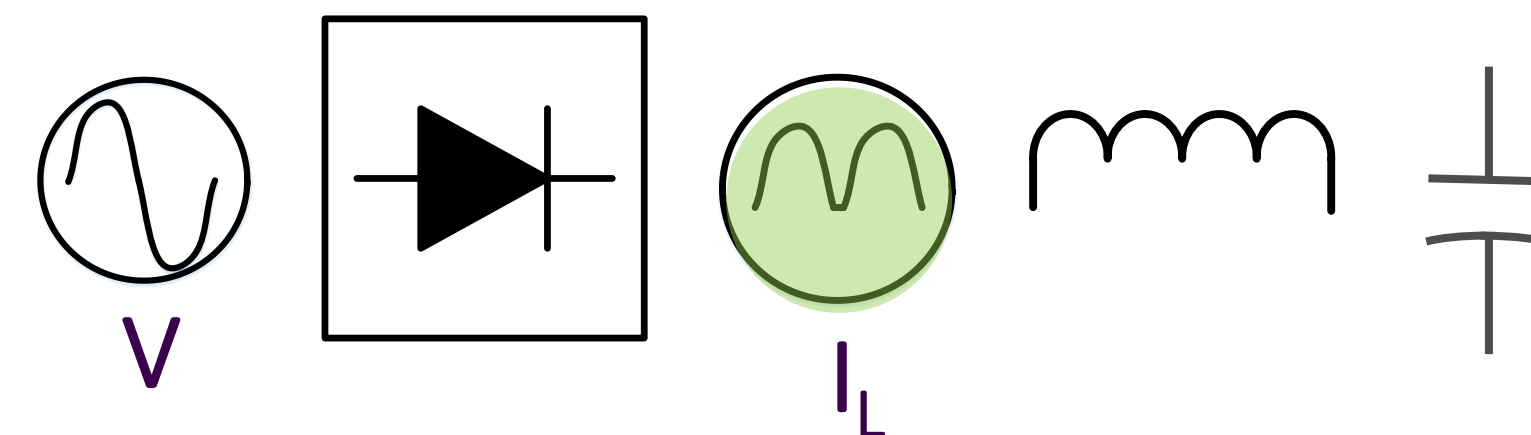

Power Factor Improvement

Boost to HV
“Bulk”
Storage
Capacitor

ULP PIEZO Research – AlN Piezo Harvester

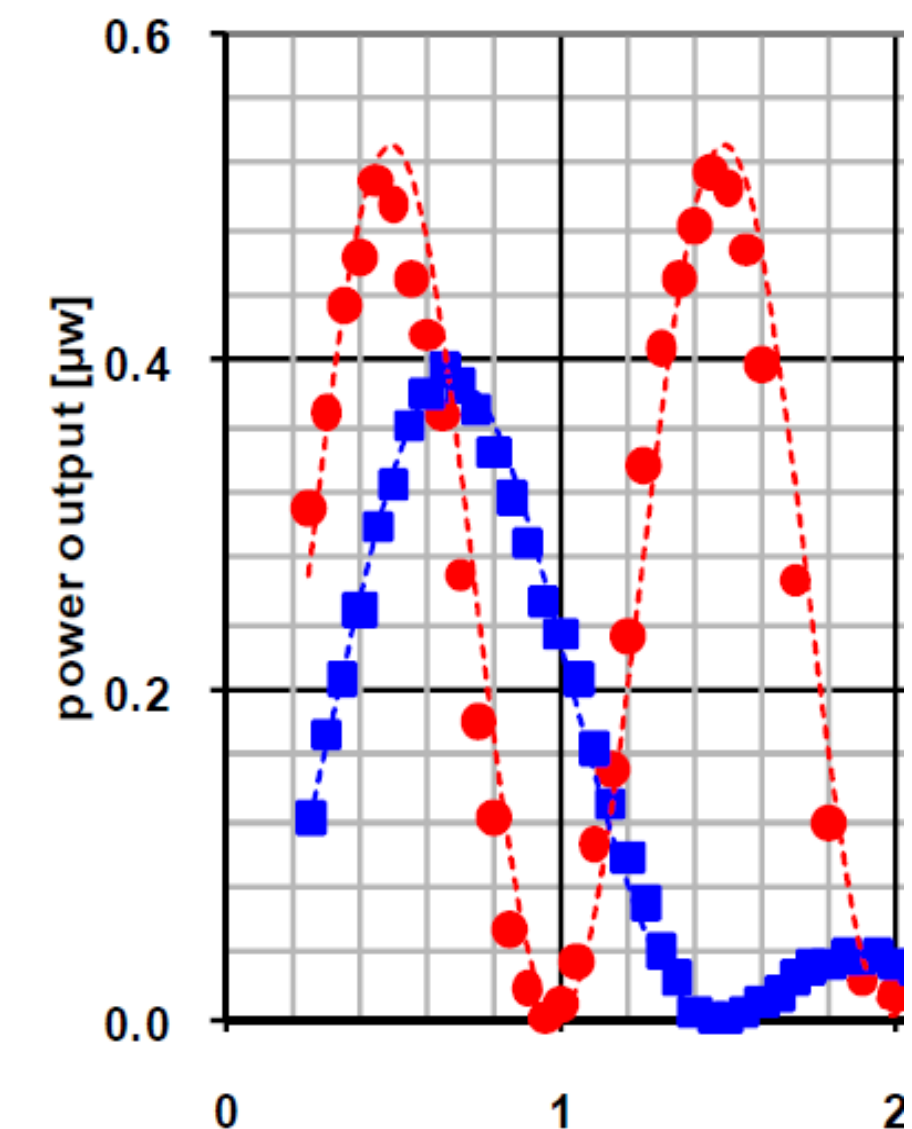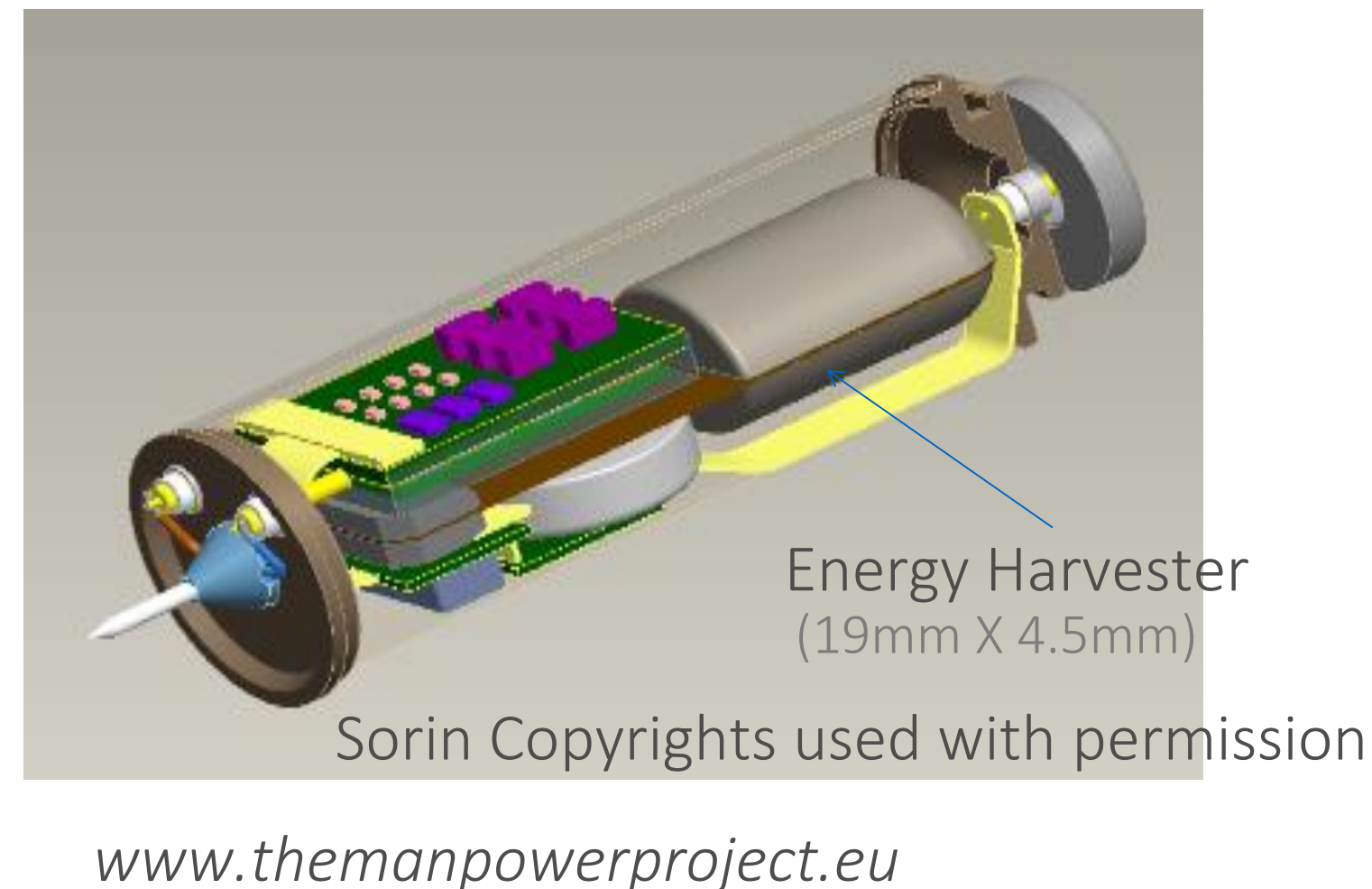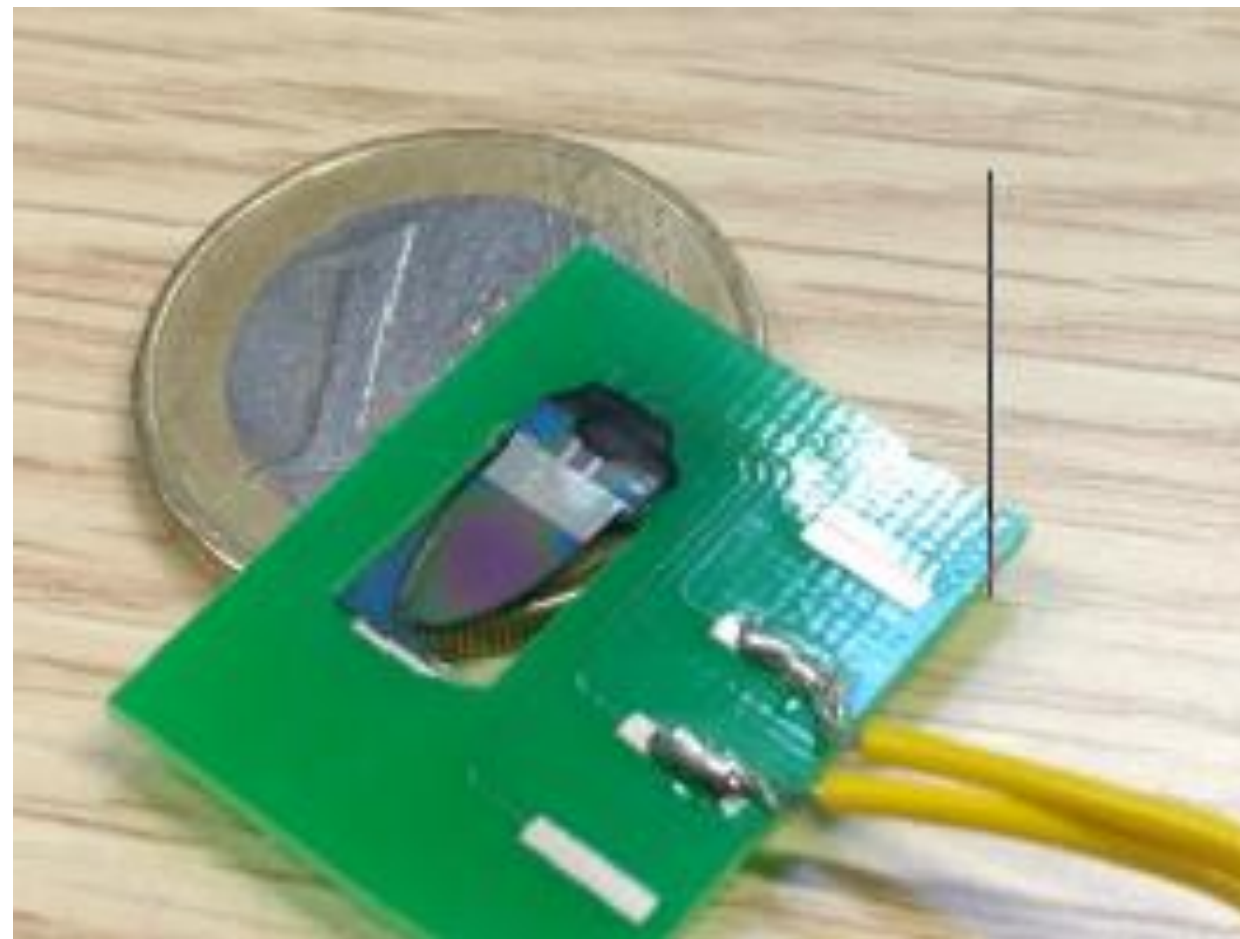

Elfrink et al.
2010

Blue: Shock
induced off
resonance

Red: At
resonance

Leadless implantable – Tyndall created the Piezo harvester – double cantilever
~3µW (1-10V) average power operating at 60 bpm, fits inside a commercial leadless pacemaker.



Off-resonance based on impulse acceleration method – MEMs compatible process

Substantial further improvements are possible and mixed signal control will add value

Maximise energy extraction during single shock excitation, as an example.

Piezo – Energy Extraction at Mechanical Vibration Frequency from a Capacitive Source

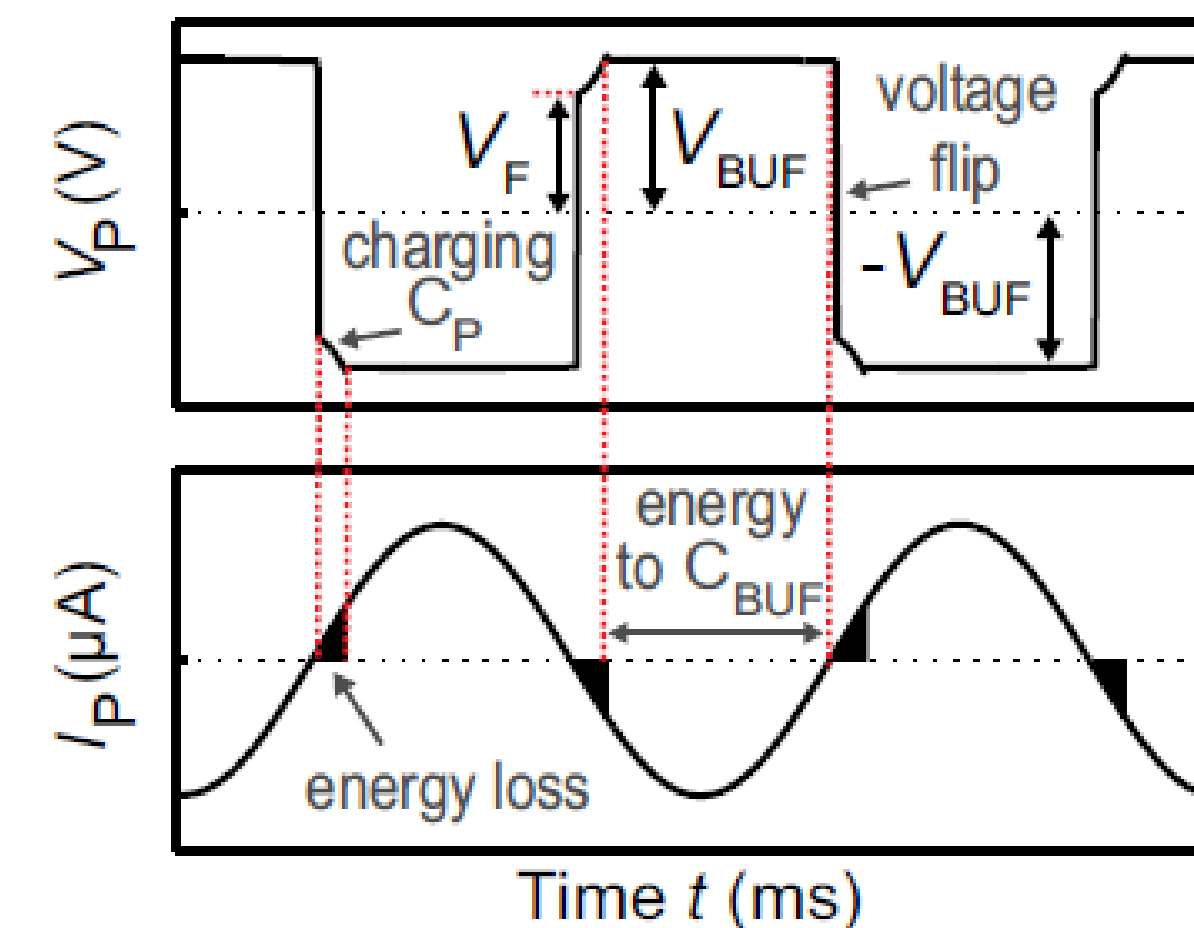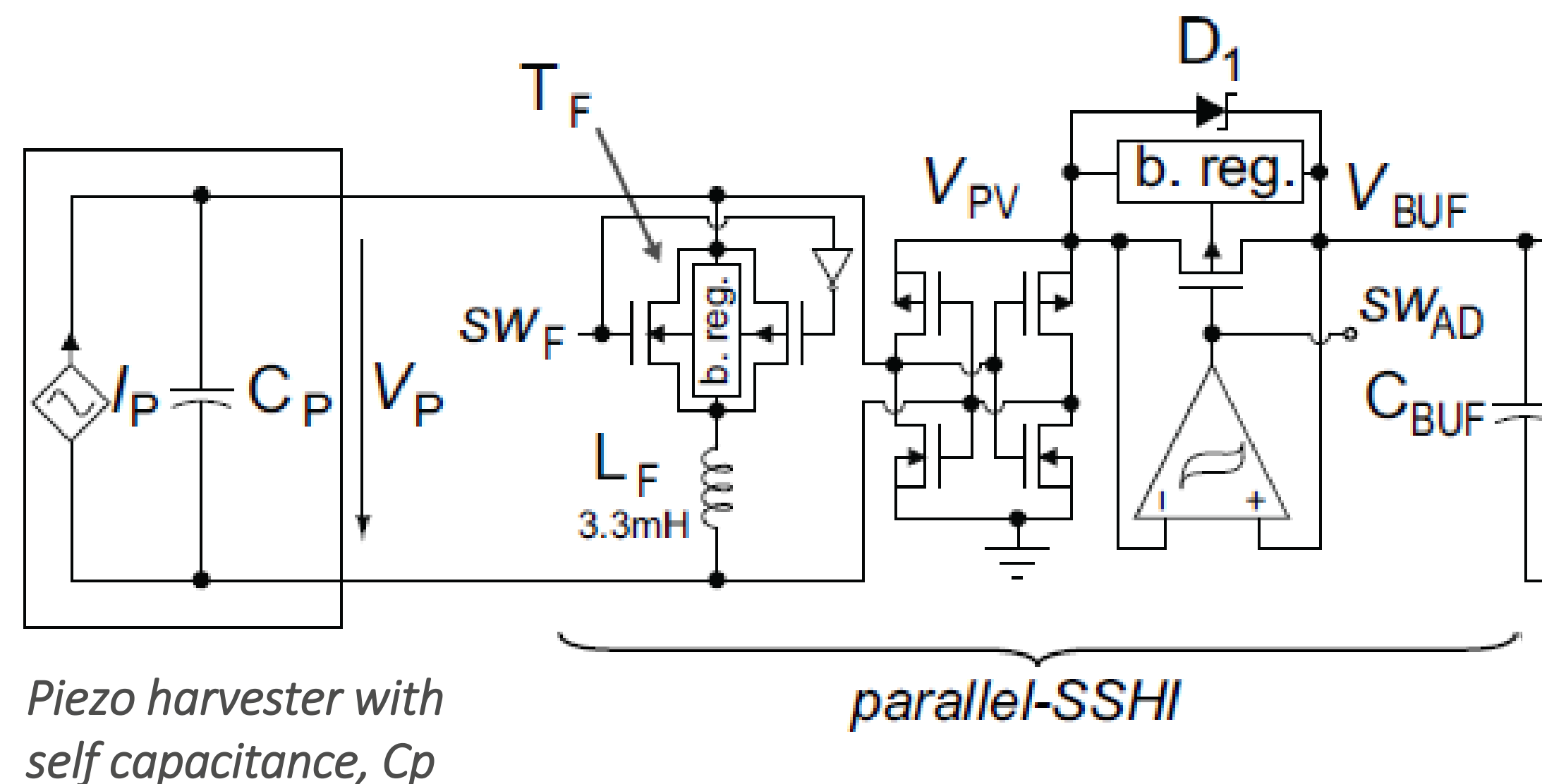- At the vibration frequency (Ω_M) – facilitates ULP
- A quickly evolving variety of Active Rectifier, Conduction Angle Extension (Bias Flip, Parallel Synchronous Switch Harvesting on Inductor (P-SSHI)) or other Synchronous Charge Extraction (SECE) techniques.



Current Source Generator results in Square Wave Voltage determined by MPPT Control of DC Voltage after the rectifier

“A 4μW-to-1mW Parallel-SSHI Rectifier for Piezoelectric Energy Harvesting of Periodic and Shock Excitations with Inductor Sharing, Cold Start-up and up to 681% Power Extraction Improvement”, Daniel A. Sanchez et. al., ISSCC 2016



SECE Piezo Harvesting Circuit Example

EUROSENSORS 2014, the XXVIII edition of the conference series

Quasi-Synchronous Charge Extraction for Improved Energy Harvesting from Highly Coupled Piezoelectric Transducers

Aldo Romani*, Matteo Filippi

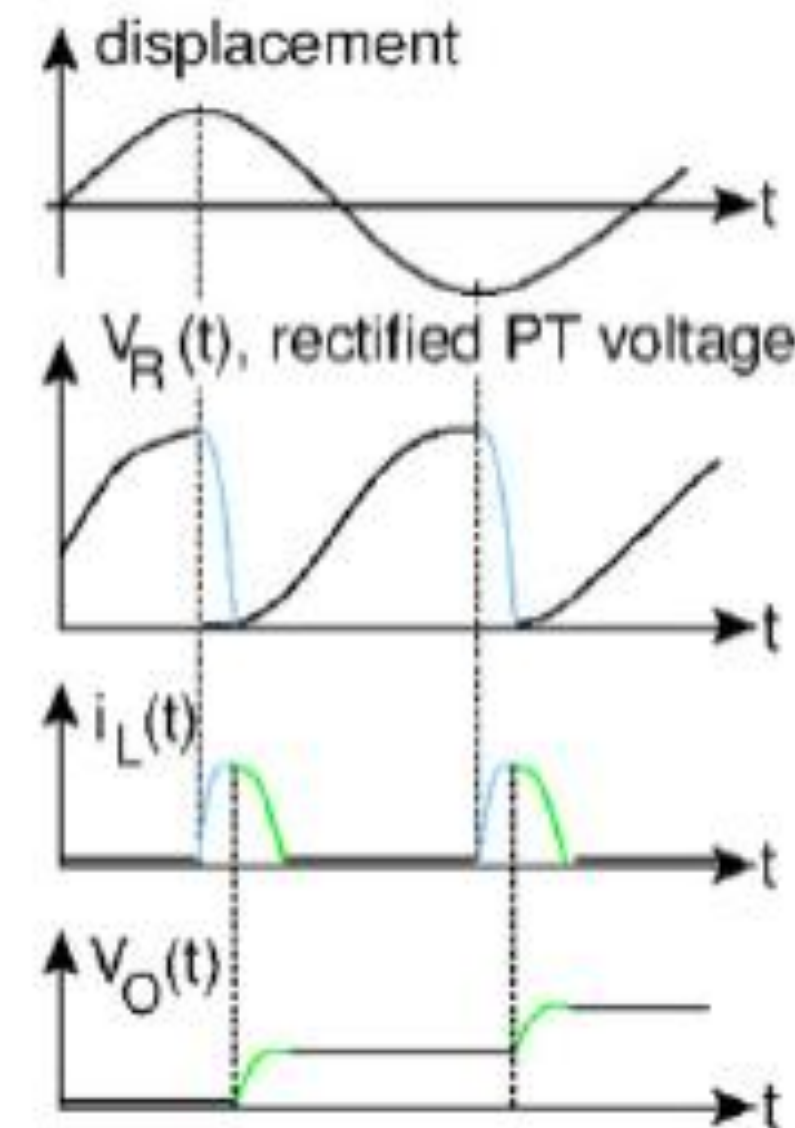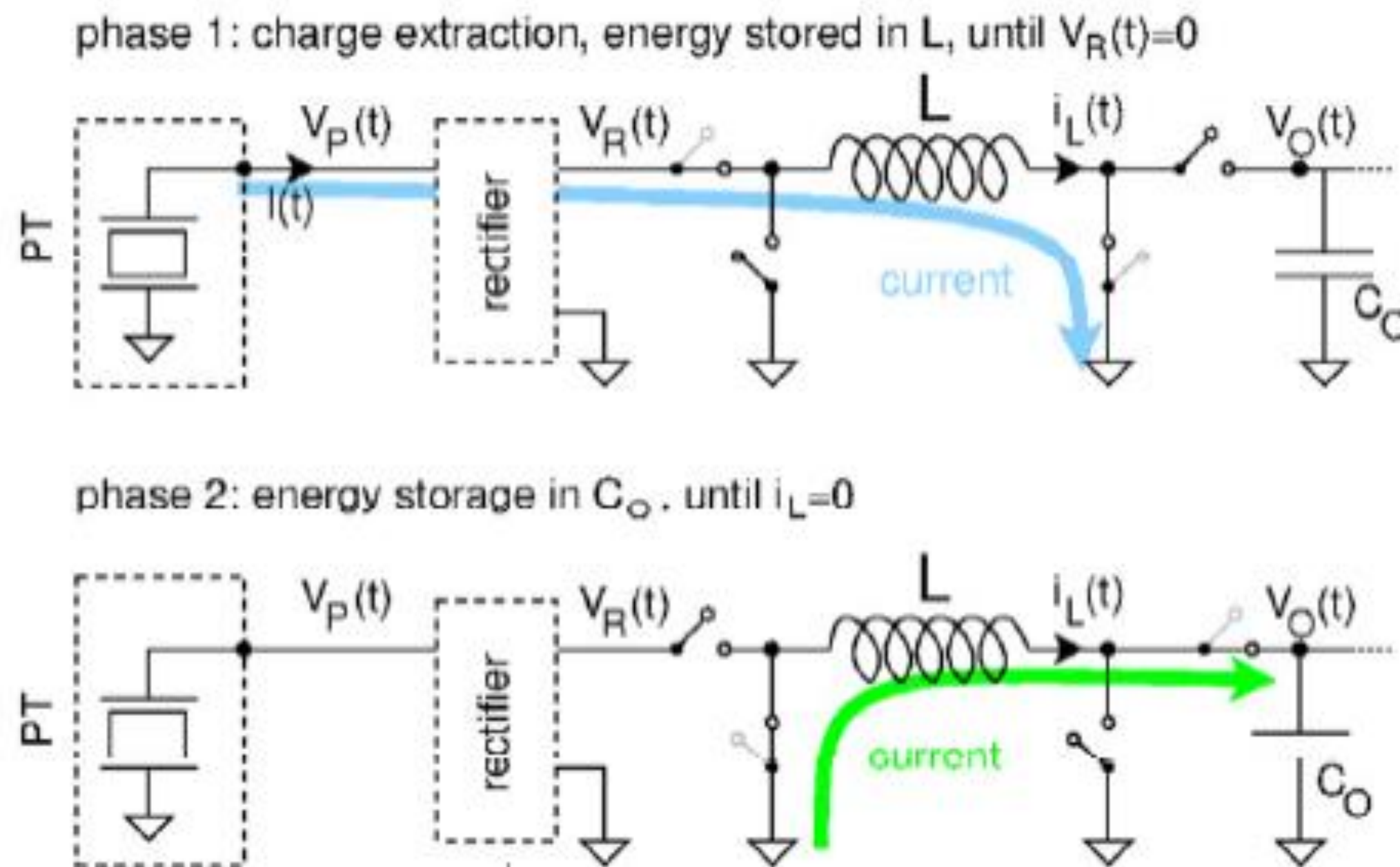University of Bologna, Via Venezia 52, Cesena 47521, Italy



This is a Buck-Boost Circuit operated synchronously with mechanical vibration to resonantly (efficiently) extract charge from the piezo capacitive source

All of these harvesting circuits benefit from:

- MPPT
- Analog Event Driven State Machines
- Digital Timing Circuits
- High Speed Low Threshold Comparators



Mechanical and Electrical Co-Design VEH

- Mechanical Non-Linearities added in transducer design +
- Non-Linear Electrical Stimuli to maintain high energy branch resonances
-
- Design for high reliability involves advanced packaging design
 - Signal interaction, such as displacement, strain measurement
 - Electrical techniques to increase reliability

“Surfing the high energy branch of nonlinear energy harvesters”, D. Mallick, S. Roy, Phys. Rev. Lett., week ending 4 NOVEMBER 2016, claim 32 X

Example for Electromagnetic VEH

There are analogous techniques for Piezo under review by IEEE MEMS

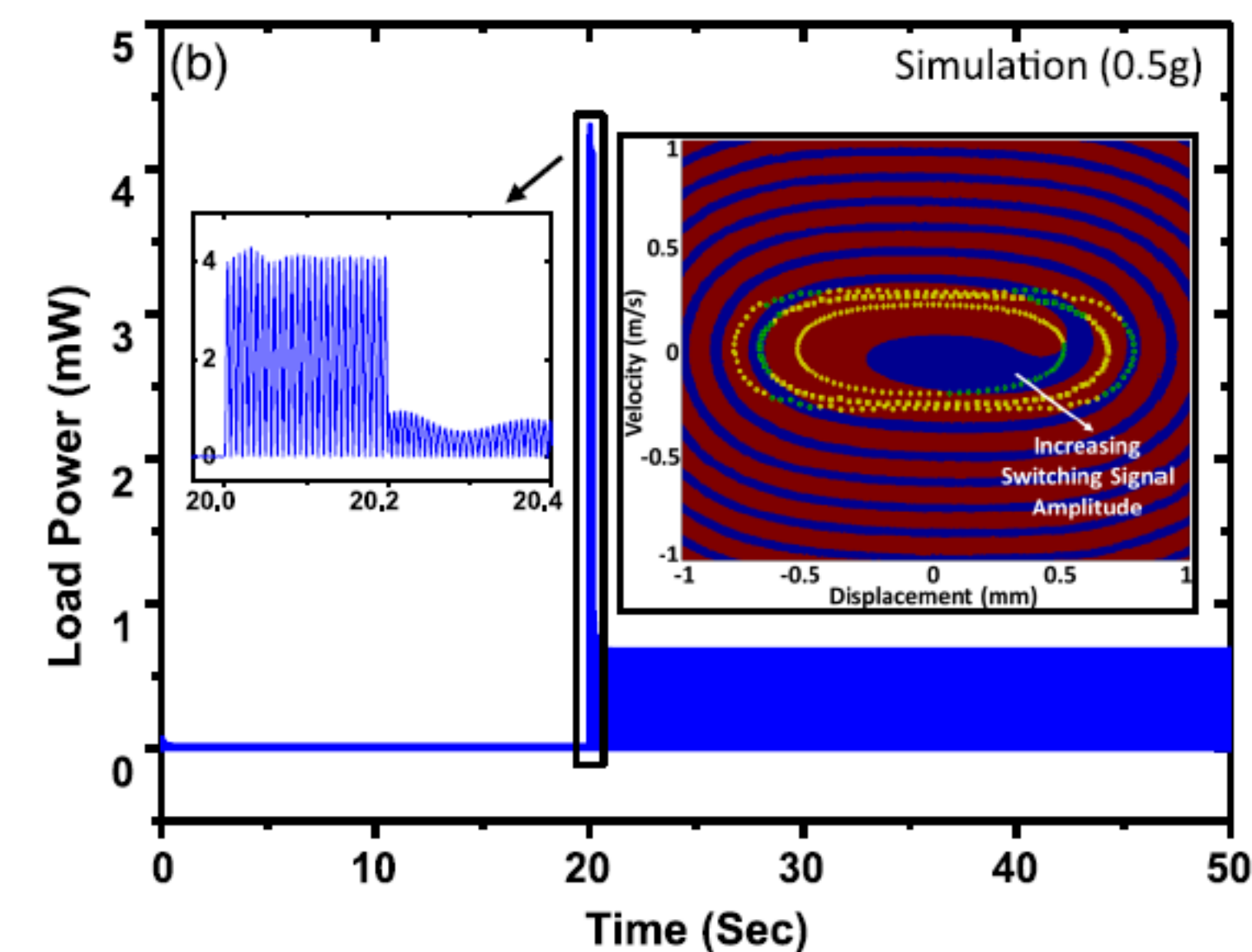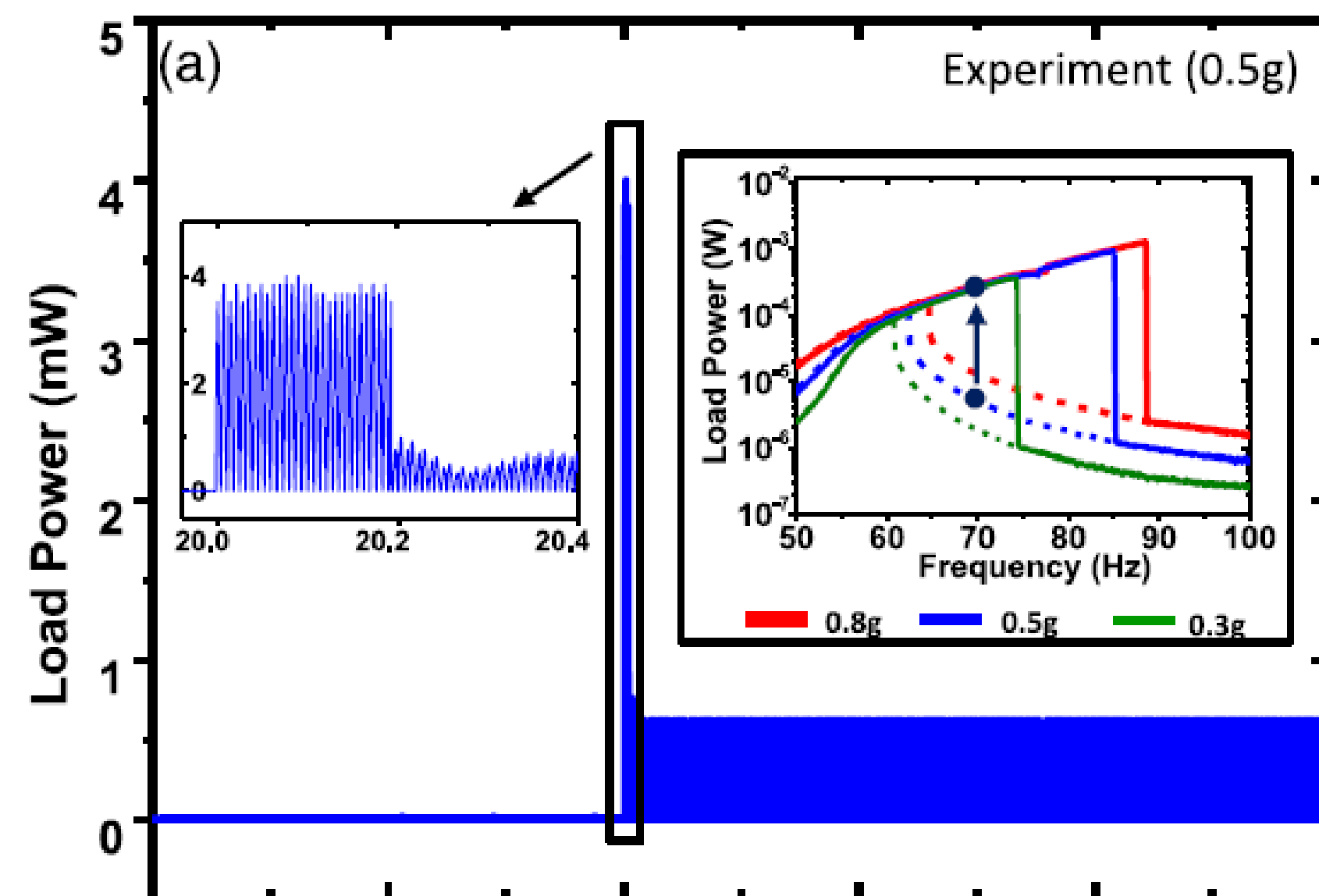


EnerHarv 2018

Platform Circuit Design Philosophy

- **Lowest Quiescent Current Blocks**, in combination with:
- **Optimised Energy Transfer per Cycle**
 - Frequency scalable or as required energy cycle transfer
 - Efficient and Linear over wide dynamic range
 - Burst Mark-Space duty cycling and optimum cycles per Burst Mark
- **Control functionality on demand – Control power \propto burst frequency**
- **Inductor based Switch Mode**
 - Efficient at processing high energy per cycle
 - Inductors are extremely compliant for wide voltage range
 - *Drawback is that large L value and low DCR (high RMS) is required*
=> “very large” 22uH+ inductor – 4 x 4 x 1.8 mm (typical) size!
- **Buck or Boost (Buck-Boost Capability) for conversion to multiple system voltages**
 - Time interleaving modes allows maximisation of efficiency and possible direct conversion to multiple system voltages
- **Very low Switching Loss for high frequency**
 - Quasi Resonant (QR) Switching achieves Zero Voltage Switching (ZVS) on Boost Switch or Buck Control Switch
- **SPI Configurability**

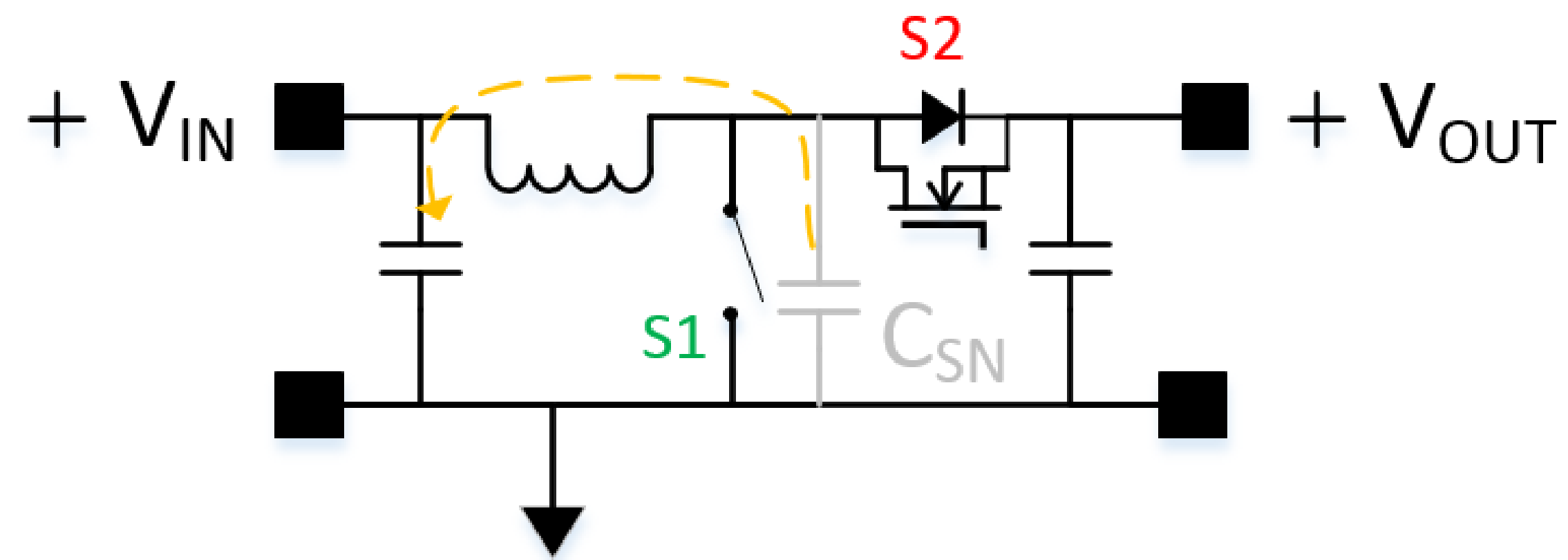Quasi-Resonance Switching for (partial) ZVS




- Resonantly ring down voltage on Switch Node parasitic capacitance, C_{SN} , (after $S2$ body diode recovers)
- Recover this into source
- Enables ZVS for lower loss
- Enables higher switching frequency, smaller size/cost

IC Process & Development Status



**0.18 Micron Modular
Trench Isolated SOI CMOS
Technology**


- **Process: XFAB 180nm**
 - Automotive, Medical and -40C-175C
 - Power, NVM & SOI options
 - High Res Poly
 - 125K gates/mm²
 - Low Sp.Ron Devices
 - 10V – 200V SuperJunction DMOS
- **3 Test Chips @ Top Level Schematic**
 - i. COLD START/ BIAS ALIVE – Layout & DRC Clean
 - ii. POWER PATH & DRIVERS – Top Level Sims
 - iii. Full Chip excluding advanced outer control loops (hysteretic only)
 - – Synthesised Verilog & Top Level Sims
- **MATLAB based *PMIC System* Design Space Exploration**
 - Complete MATLAB models match top level Cadence Simulations

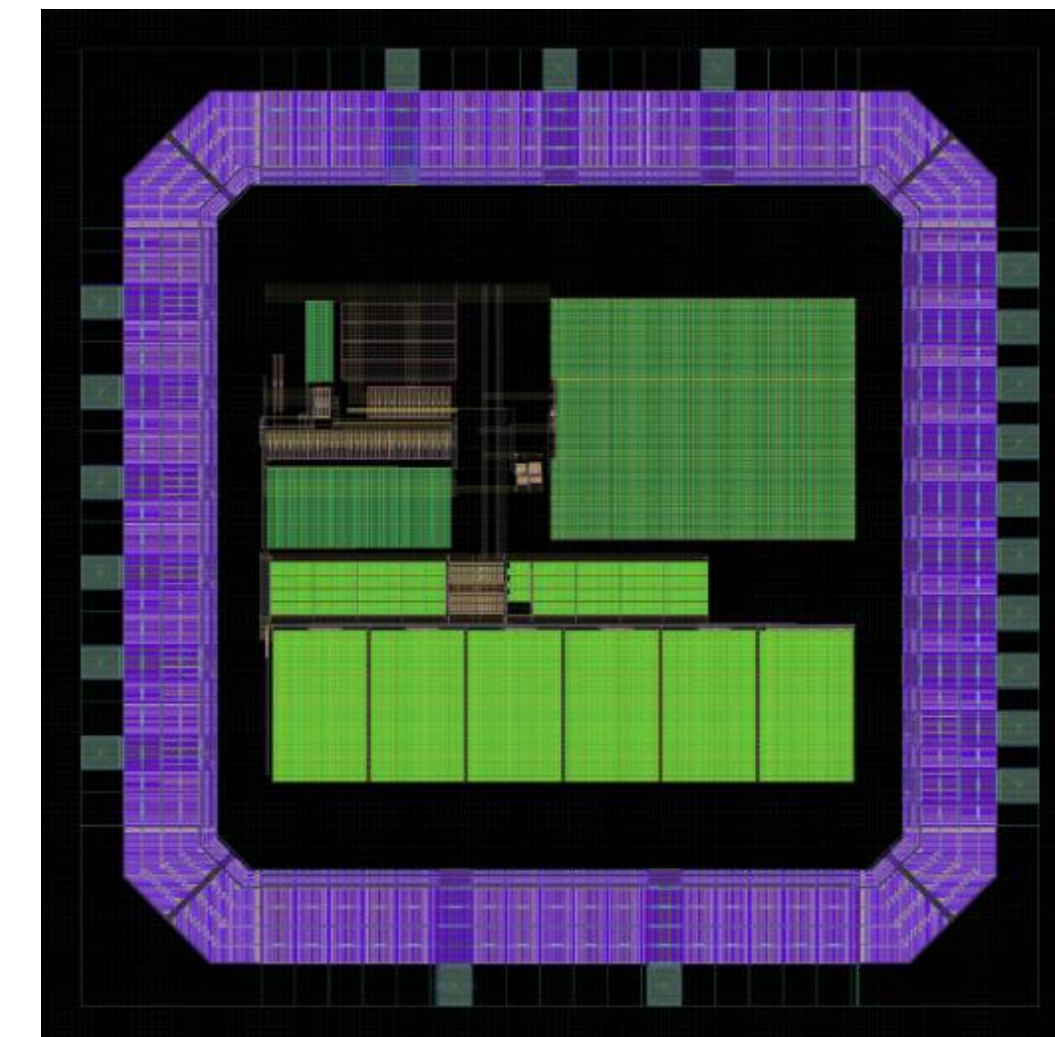

EnerHarv 2018




Mischief Platform IC

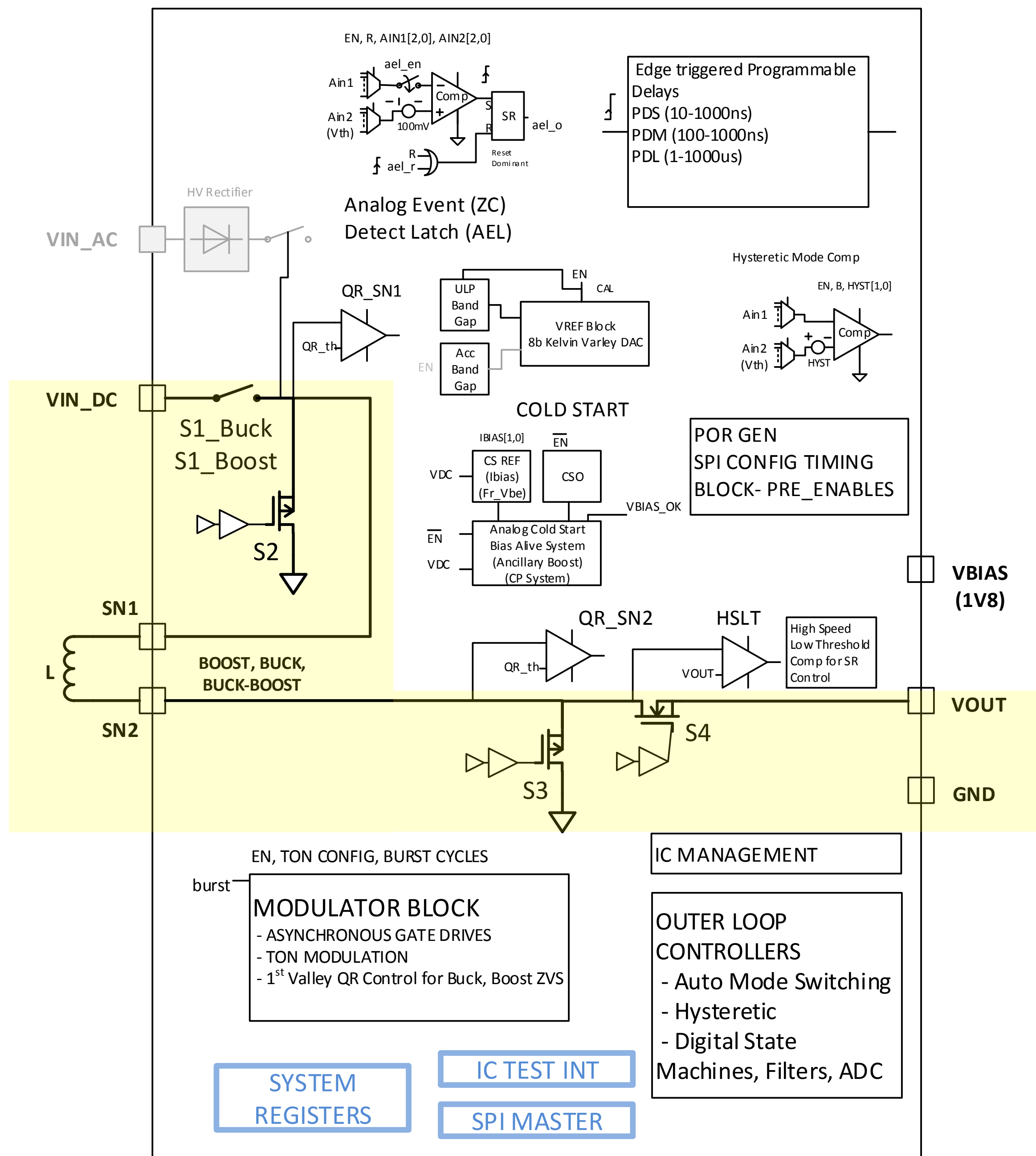

- $C_{in}=1\mu F+$, $C_{out}=10\mu F+$, $L=22\mu H$
- SPI
- Power Path 0.1mm^2
- $V_{in_DC}= 0.05 - 4V5$
- $V_{in_AC}=50V$ RMS (capable)
- $V_{out} = 1V - 4V5$
- $1\mu W - 50mW$
- $I_Q = 200\text{ nW}$ (Quiescent Power)




4-Switch Buck-Boost Converter (Non Inverting) – Design Process

- Operating in Boost or Buck Mode – More efficient than Buck-Boost Mode
- or time interleaved
- “Typical Application” of 1V5 to 3V3 chosen for Boost – Resonant Ring will give ZVS on S3
- Initial Switch Resistances chosen for Conduction Loss $\sim 3\%$
- Analytical Models and Cadence used to find initial T_{ON} for maximum efficiency {1V5, 3V3, 22 μ H inductor}
- Cadence Parametric Sweep based *Design Space Exploration* by adjusting W ($R_{DS_{on}}$) for all Switches and Drivers to further increase efficiency.

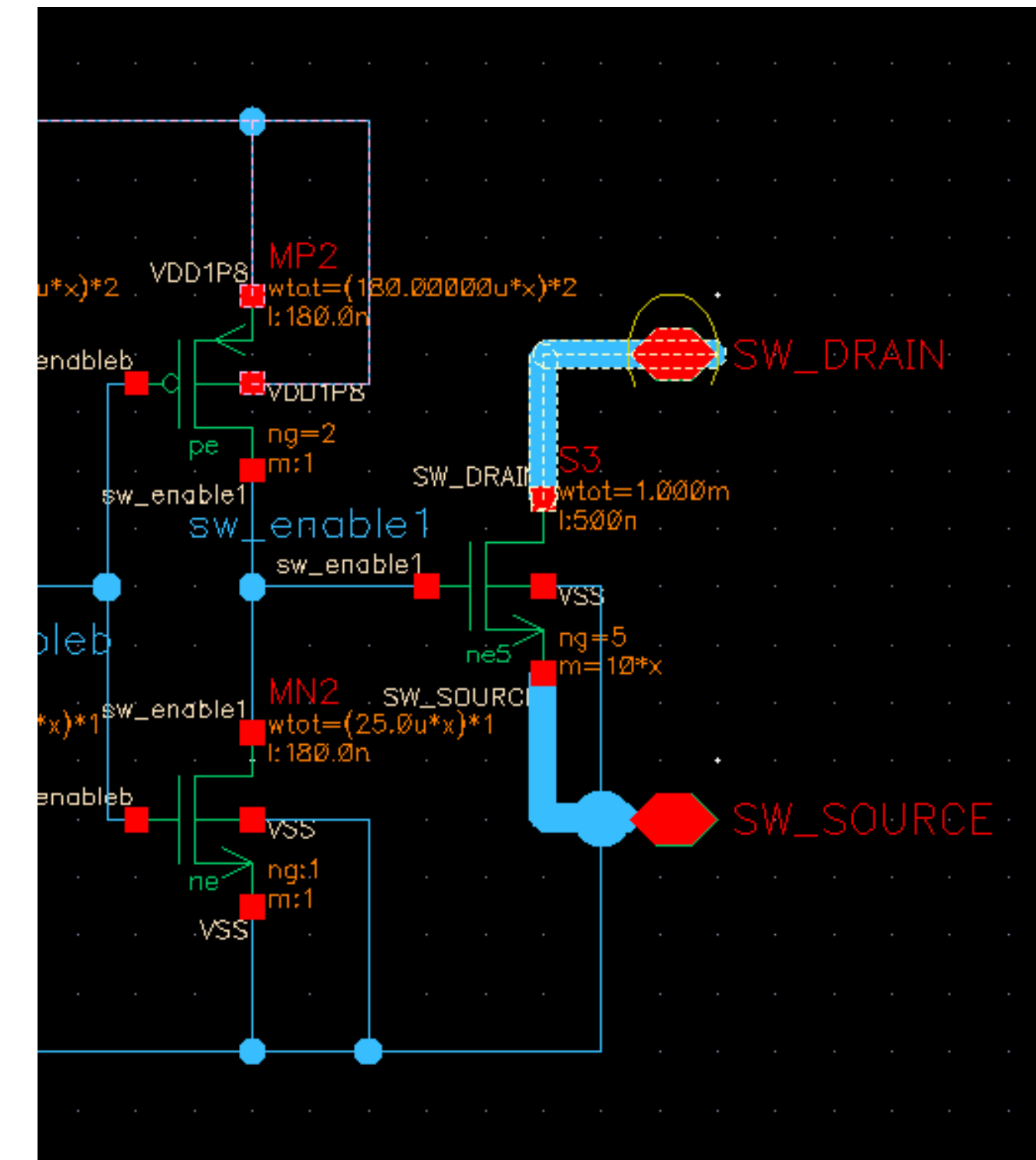


MATLAB Modelling versus Cadence Top Level Simulations

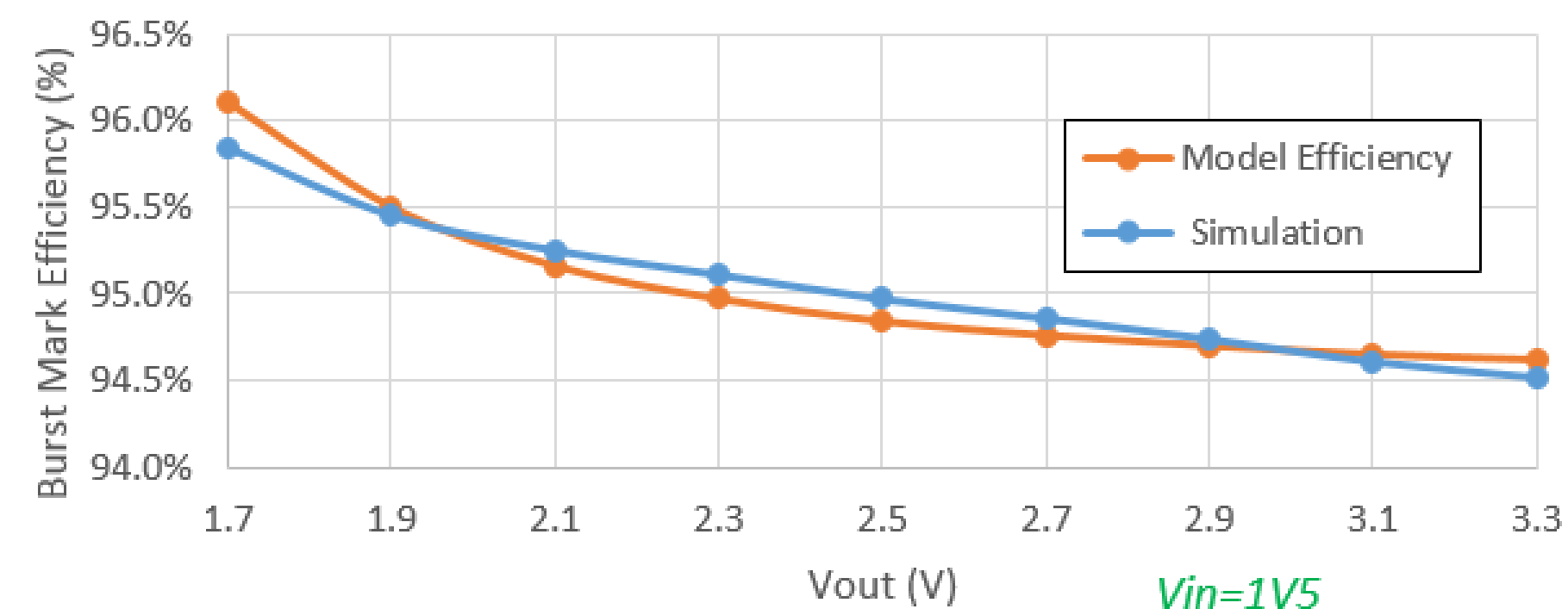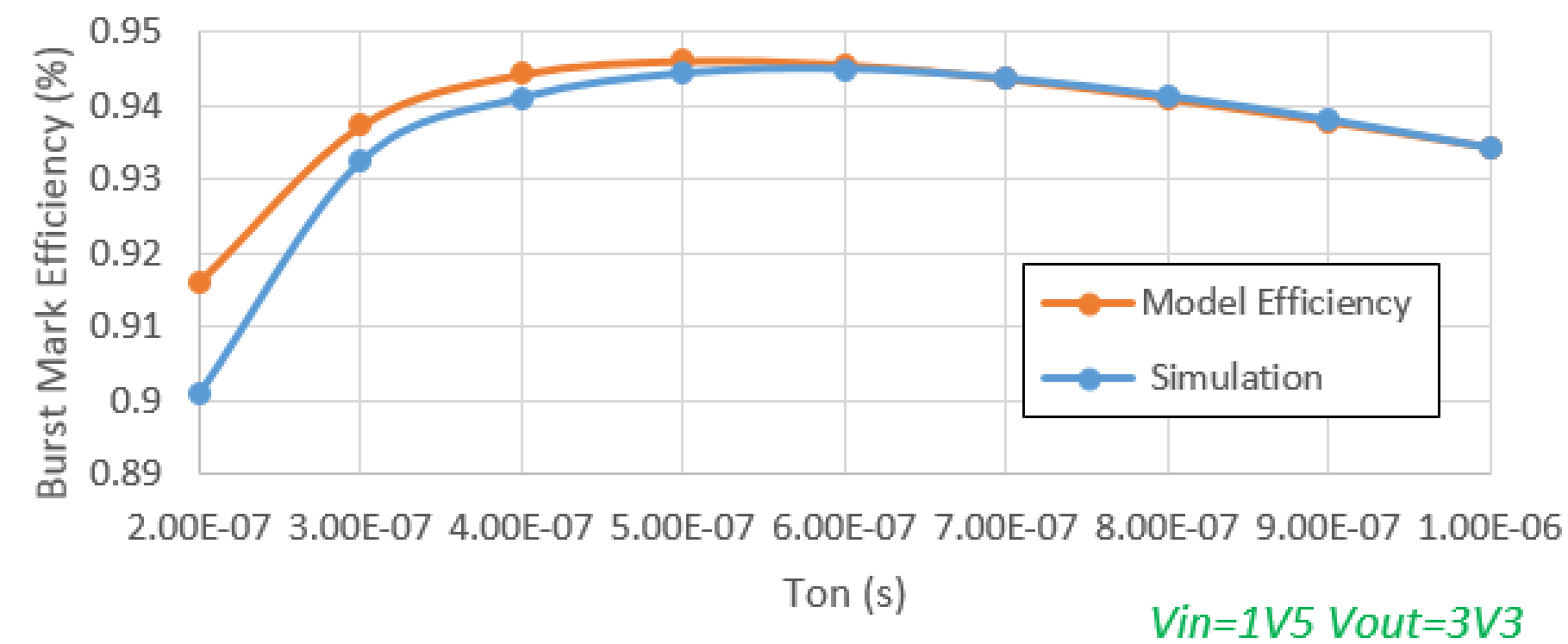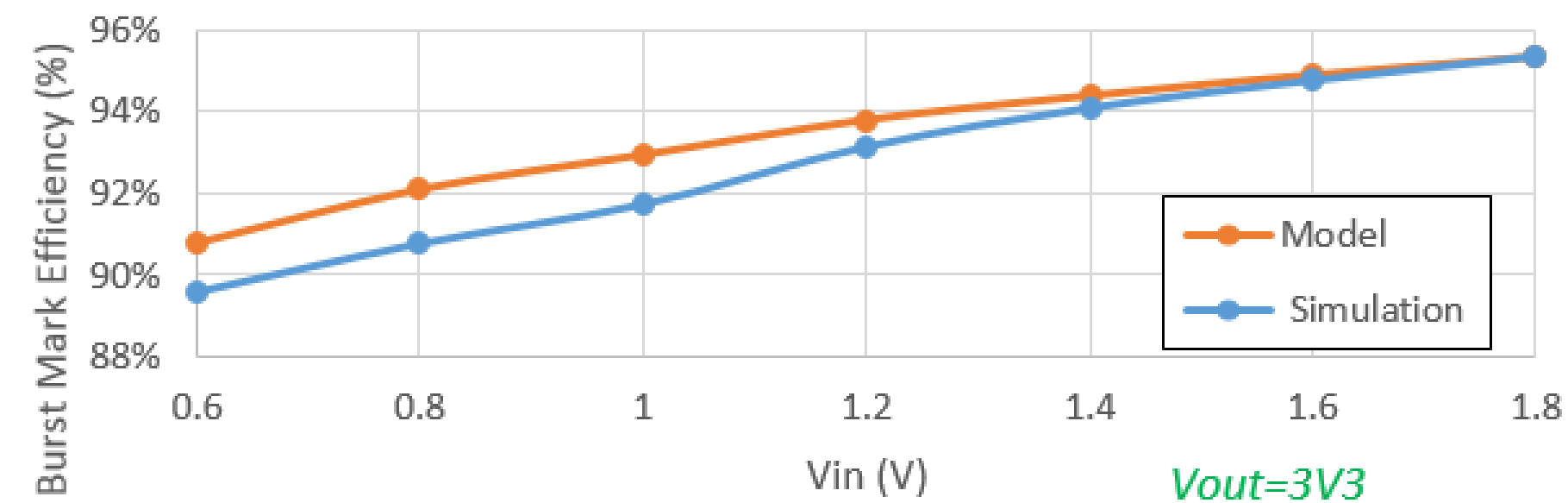Boost Mode 4 - Model vs. Simulation ($V_{out}=3.3$)




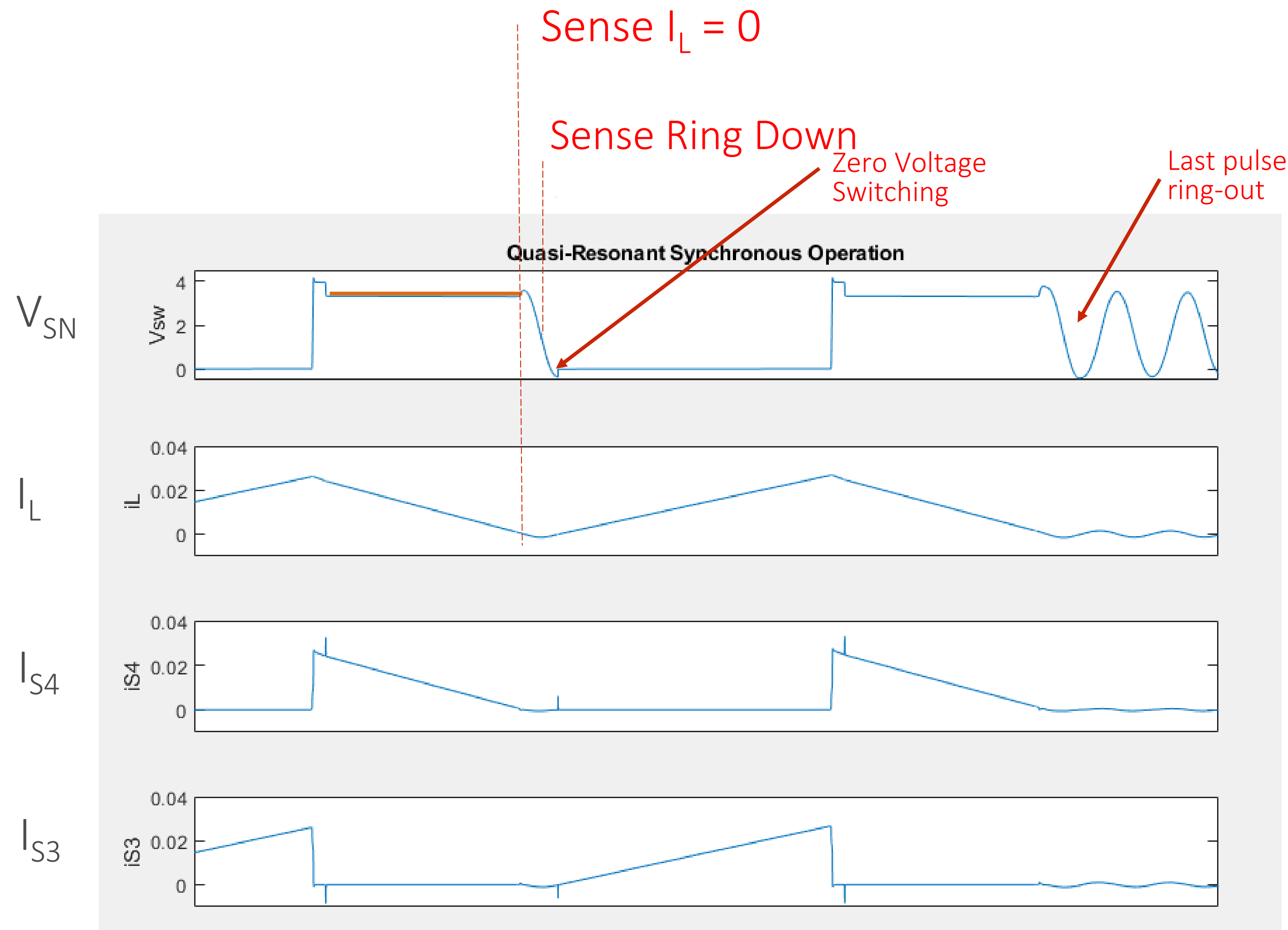
Cadence Power Path Simulations – Final 2 Pulses in Burst



Free running
Waveforms generated by
asynchronous digital state
machines controlling event
triggered analog latches

Design Process:

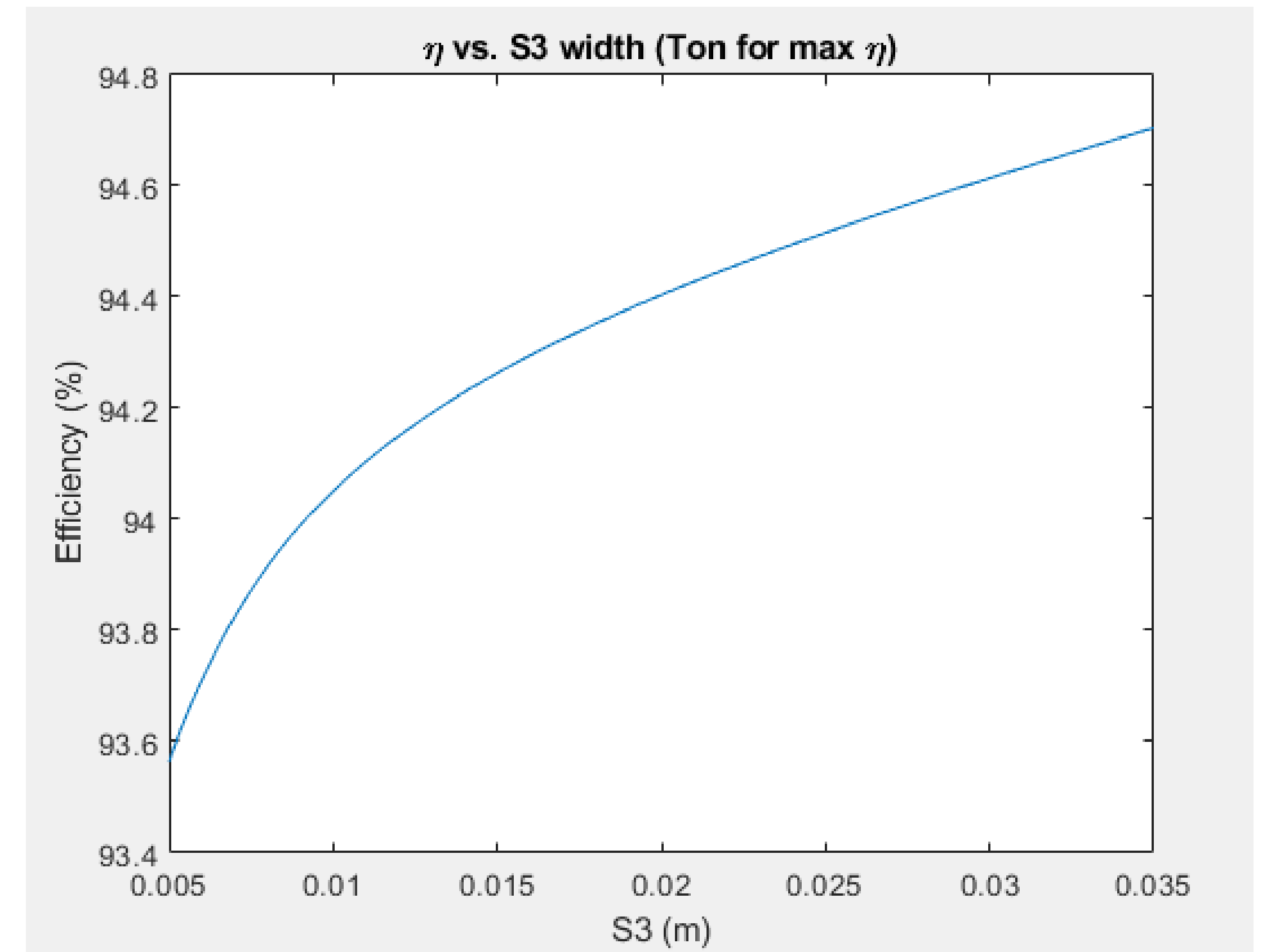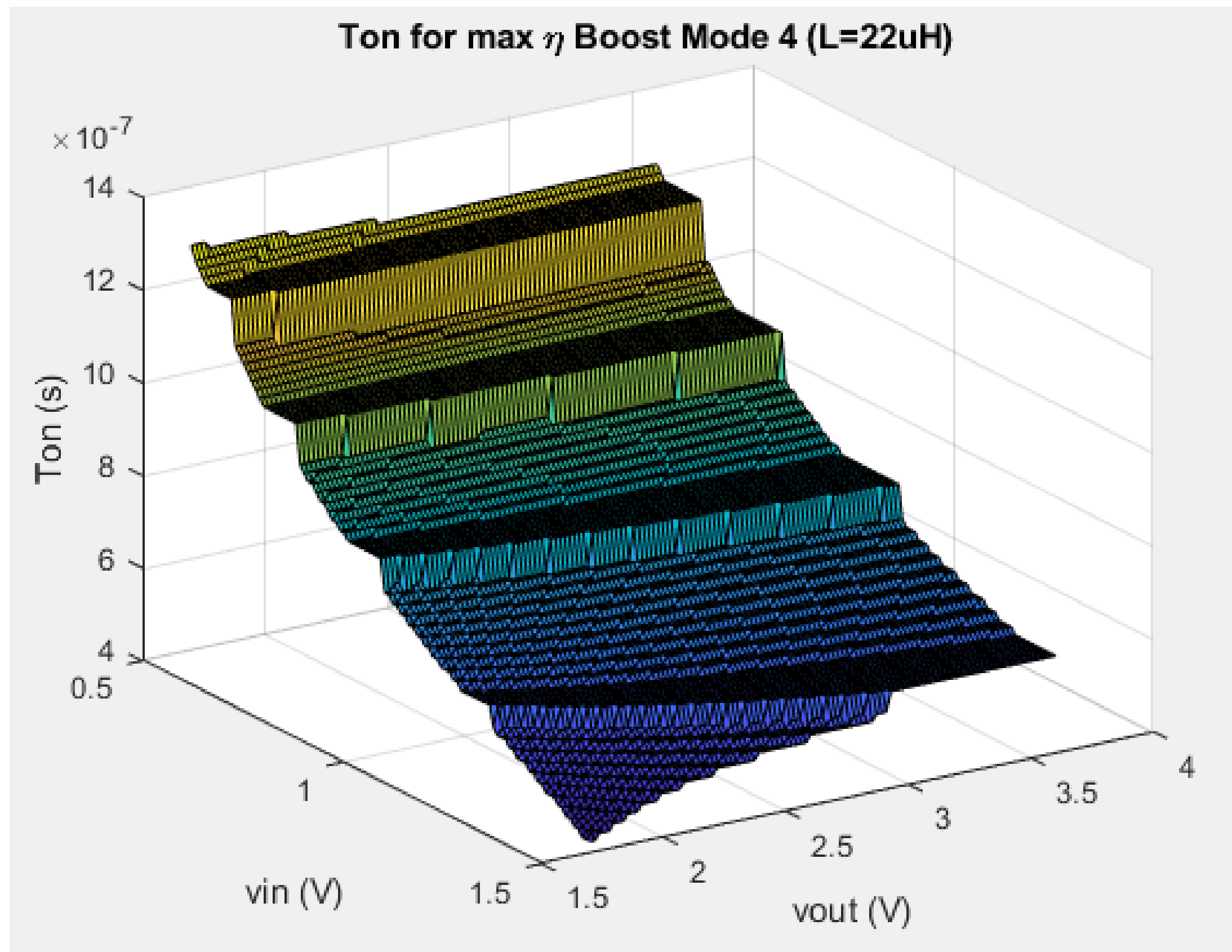
Analytically determine optimum T_{ON} Cadence Parametric Sweeps on all power path components to maximise $\eta\%$



5×10^4 Dynamic Range in Pout with Ton set for maximum efficiency


$$P_o \propto f_{BURST}$$

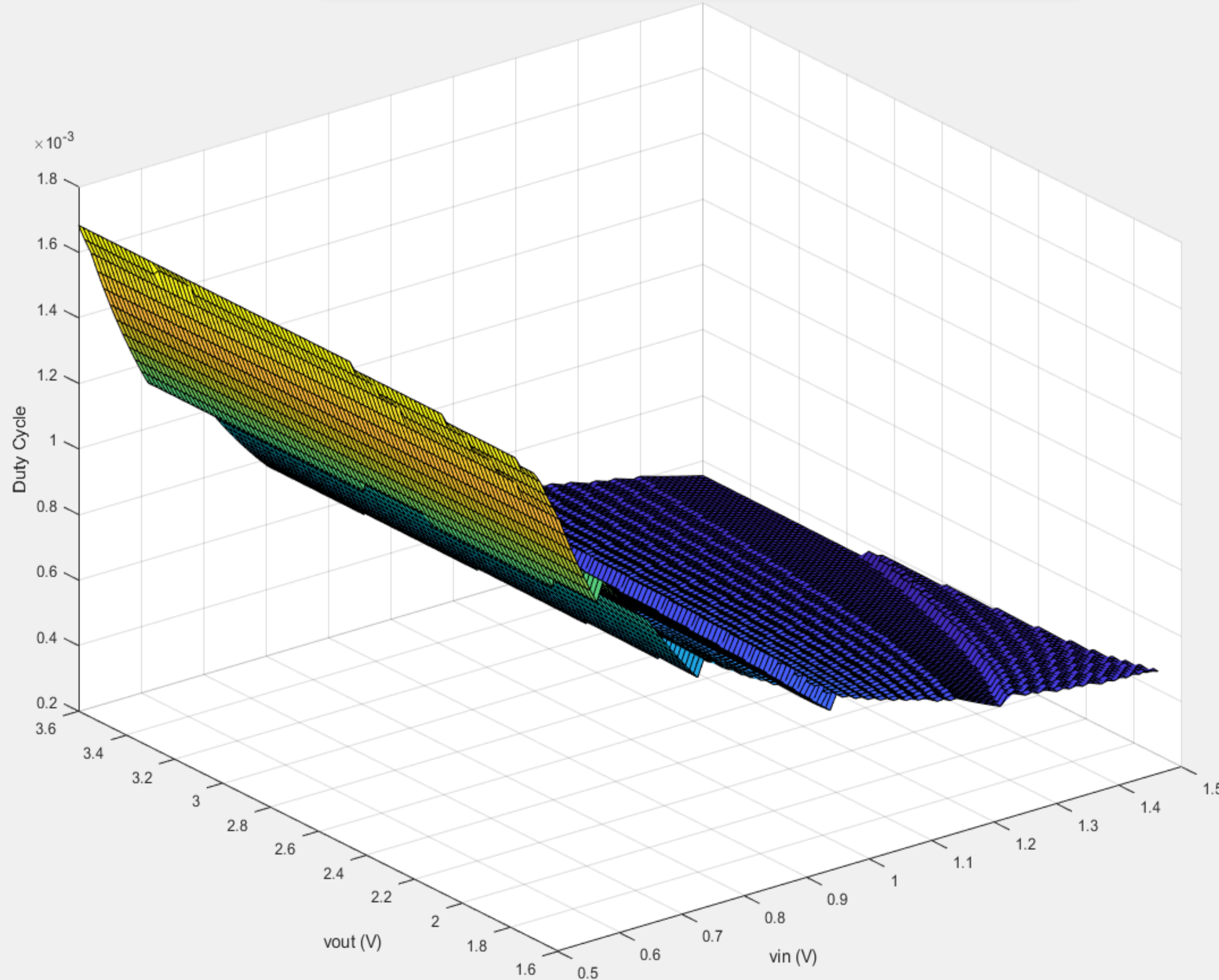D_{BURST} @ $10\mu W$ with (T_{on} for max η)



- Extend T_{on} or switch in parallel switches for larger dynamic range
- $10\mu F$ $C_{out} \Rightarrow V_{out}$ Ripple $\sim 0.25\%$
- $D_{BURST} = 0.0003$ @ $10\mu W$
- DCM (QR), ZCS, ZVS

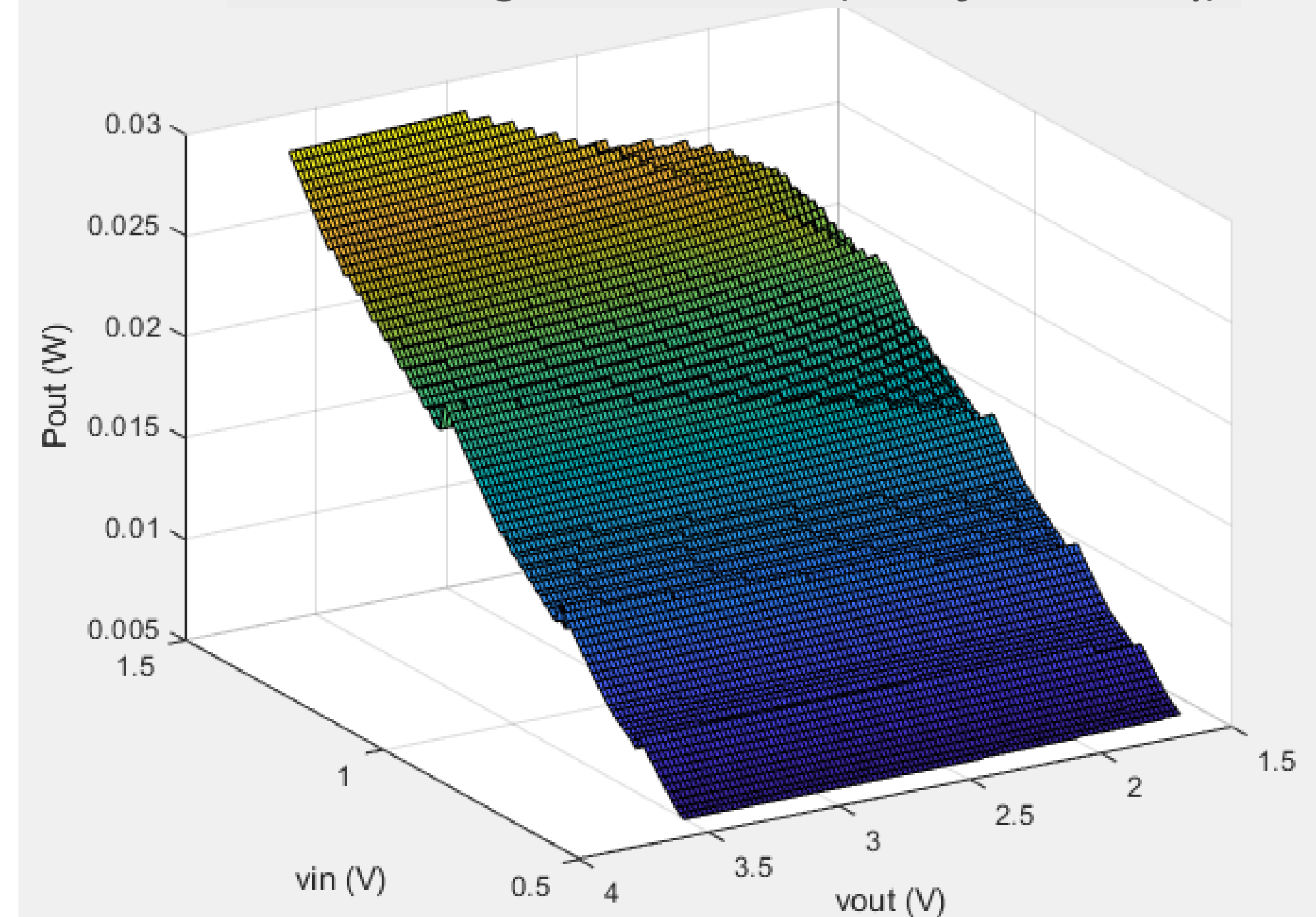
P_{out} during Burst Mark (T_{on} for max η)




Digital Assisted Analog

Configuring: Comparator Speed and Thresholds

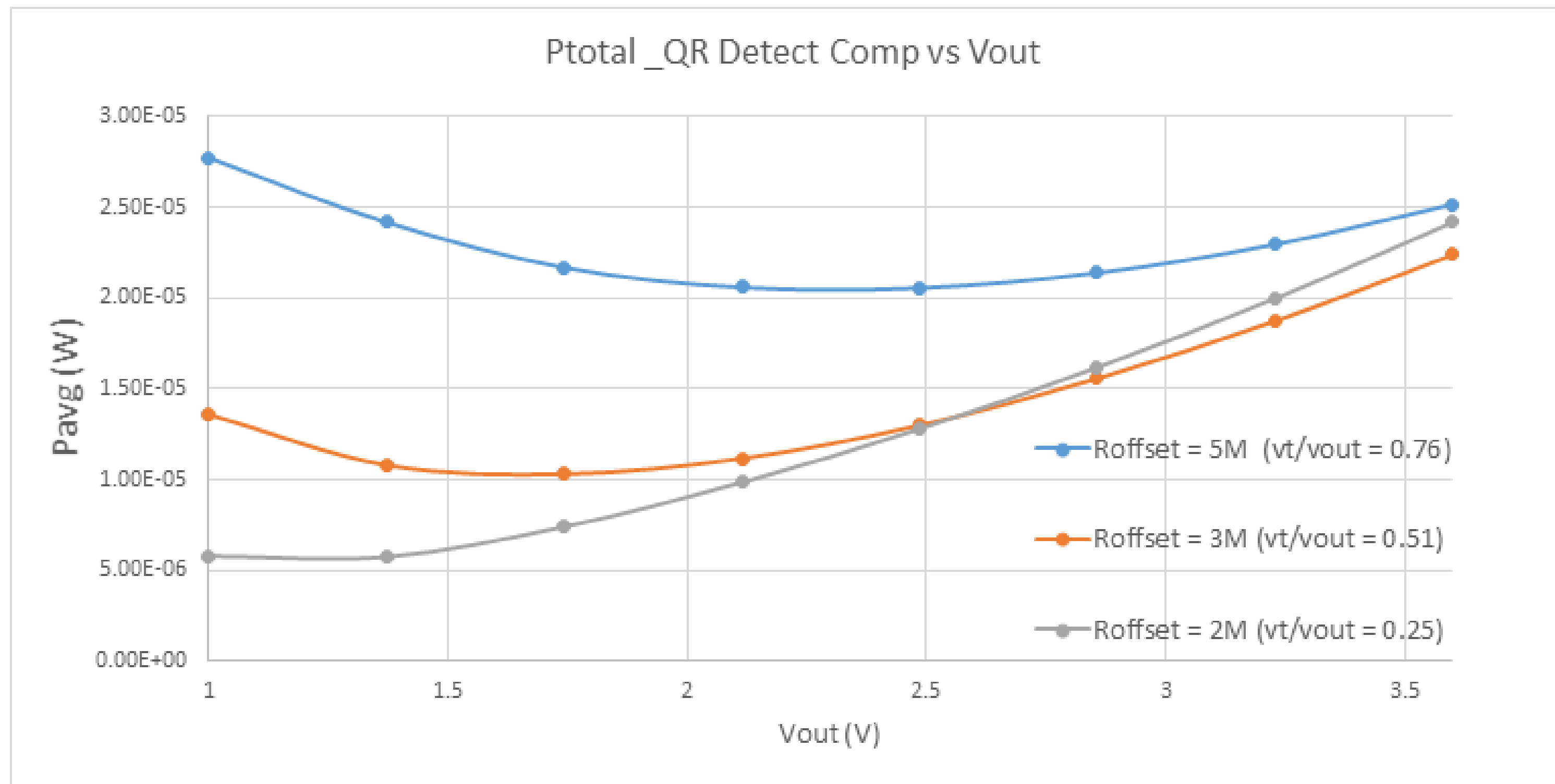- $V_{in} \sim (V_{out} + V_{rectifier}) \Rightarrow$ low $di/dt \Rightarrow$ long regions passing through HSLT or QR COMP transitions
- Separating comparator thresholds by configuration gives a 3X benefit in block consumption
- Almost all low power circuits have a configurability benefit



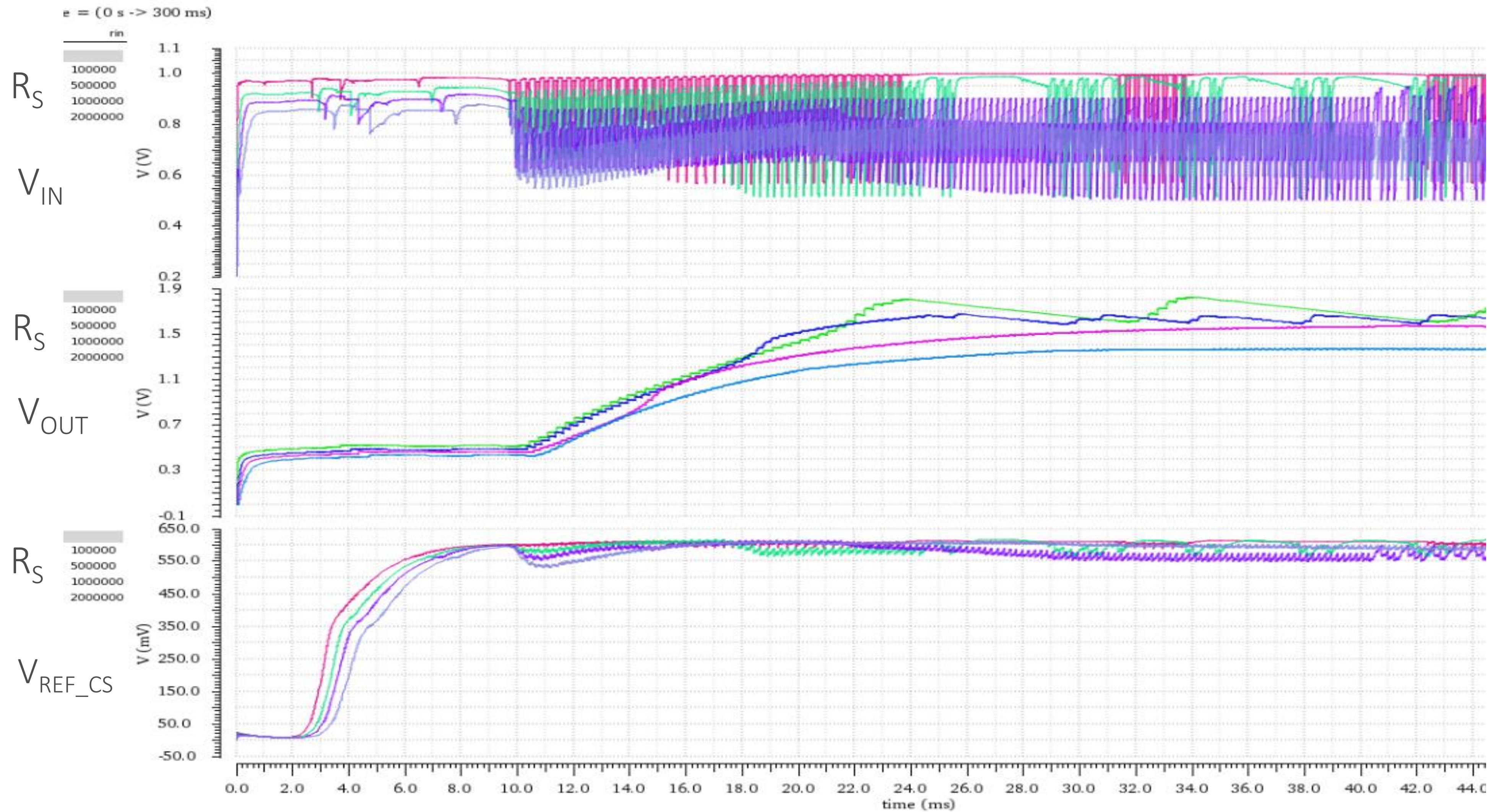Cold Start Block: Start-Up with $V_{in}=1V$, R_{SOURCE} 100k Ω – 2M Ω



2-16nA I Bias Gen

1kHz Osc

Charge Pump

Fractional BG


DAC

Comparator

Total Current = ~60nA


$V_{START} \sim 0.45V$

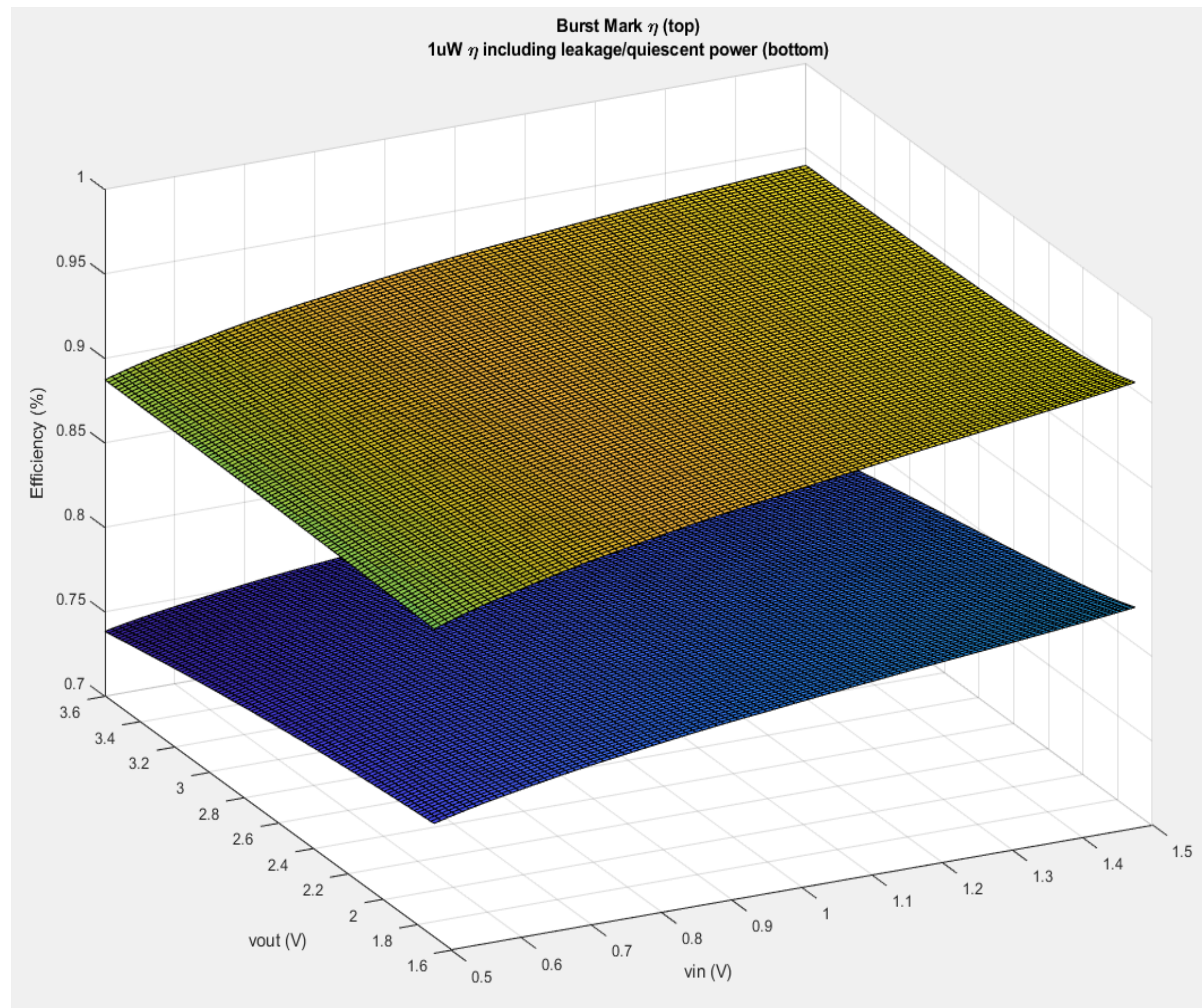Power Path Efficiency @ $1\mu\text{W}$ = 95%




Burst Duty Cycle (independent of pulses per burst)

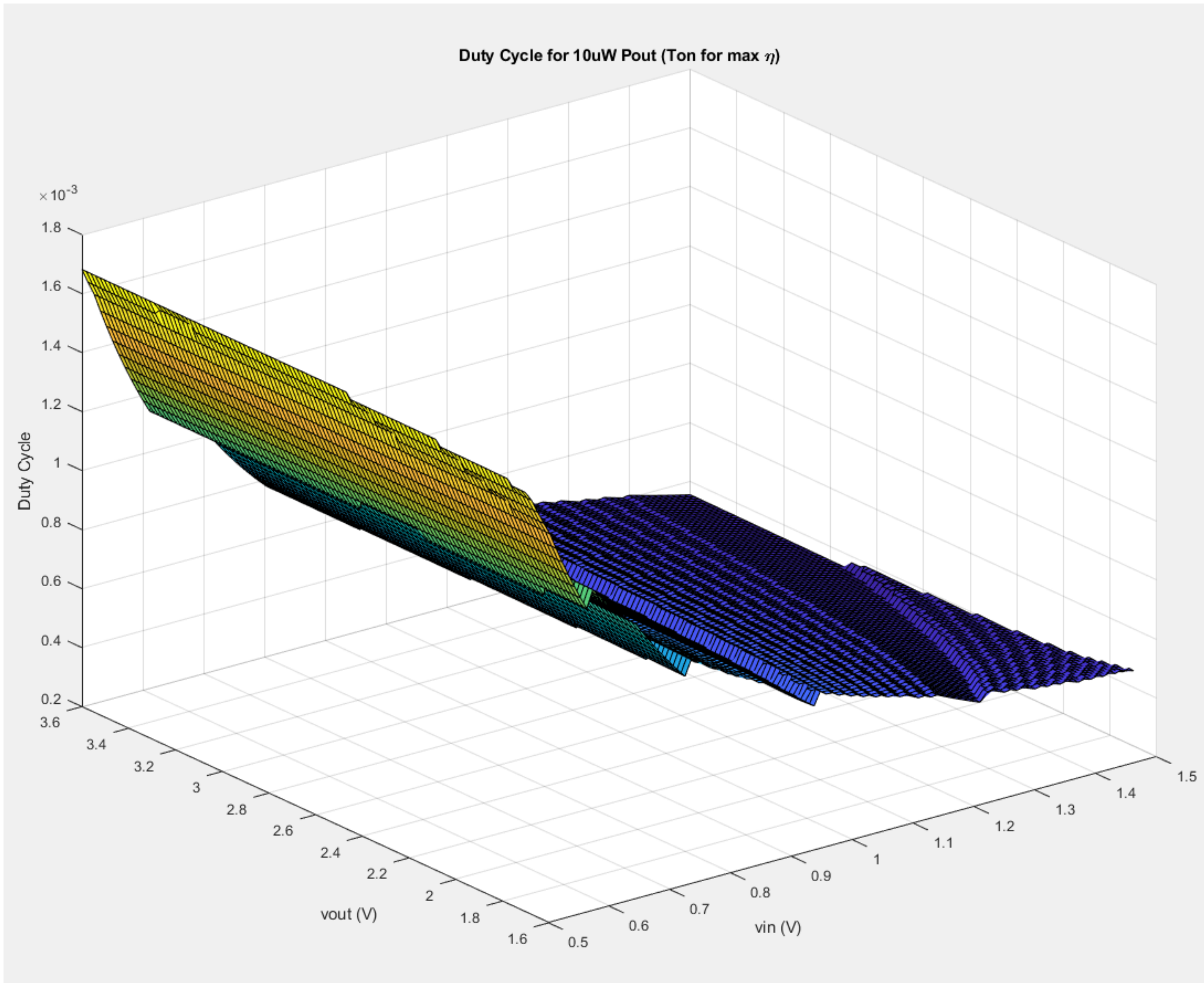- $P_o = 10 \text{ uW}$
- $D = 1 \text{ in } 1000$




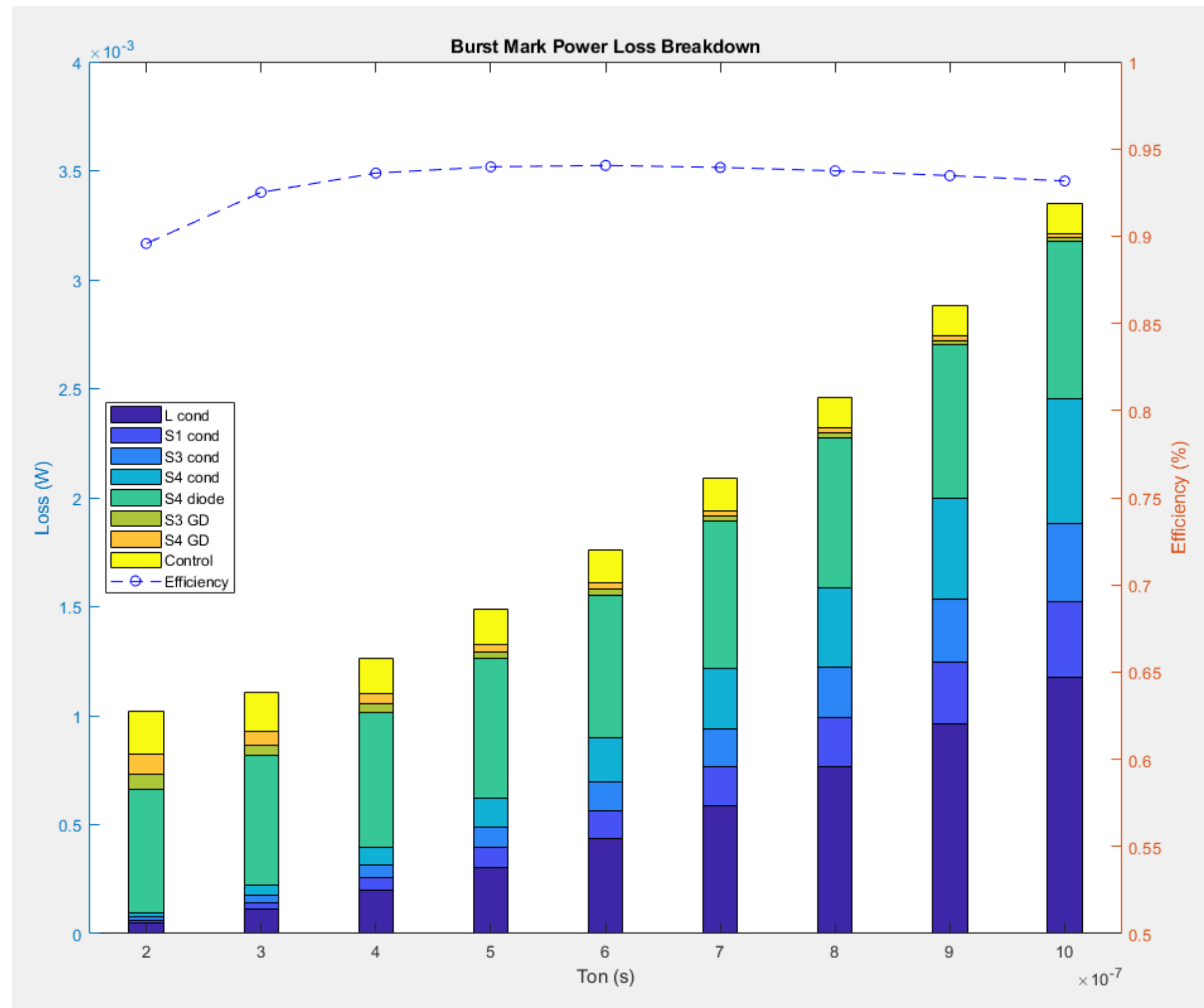10uW, 1V5-3V3, 22uH Burst Mark Power & Efficiency vs Ton



- S1-S4 Switching Loss is very low
- S4 Body Diode Conduction could be designed out
- There is opportunity to remove the large inductor


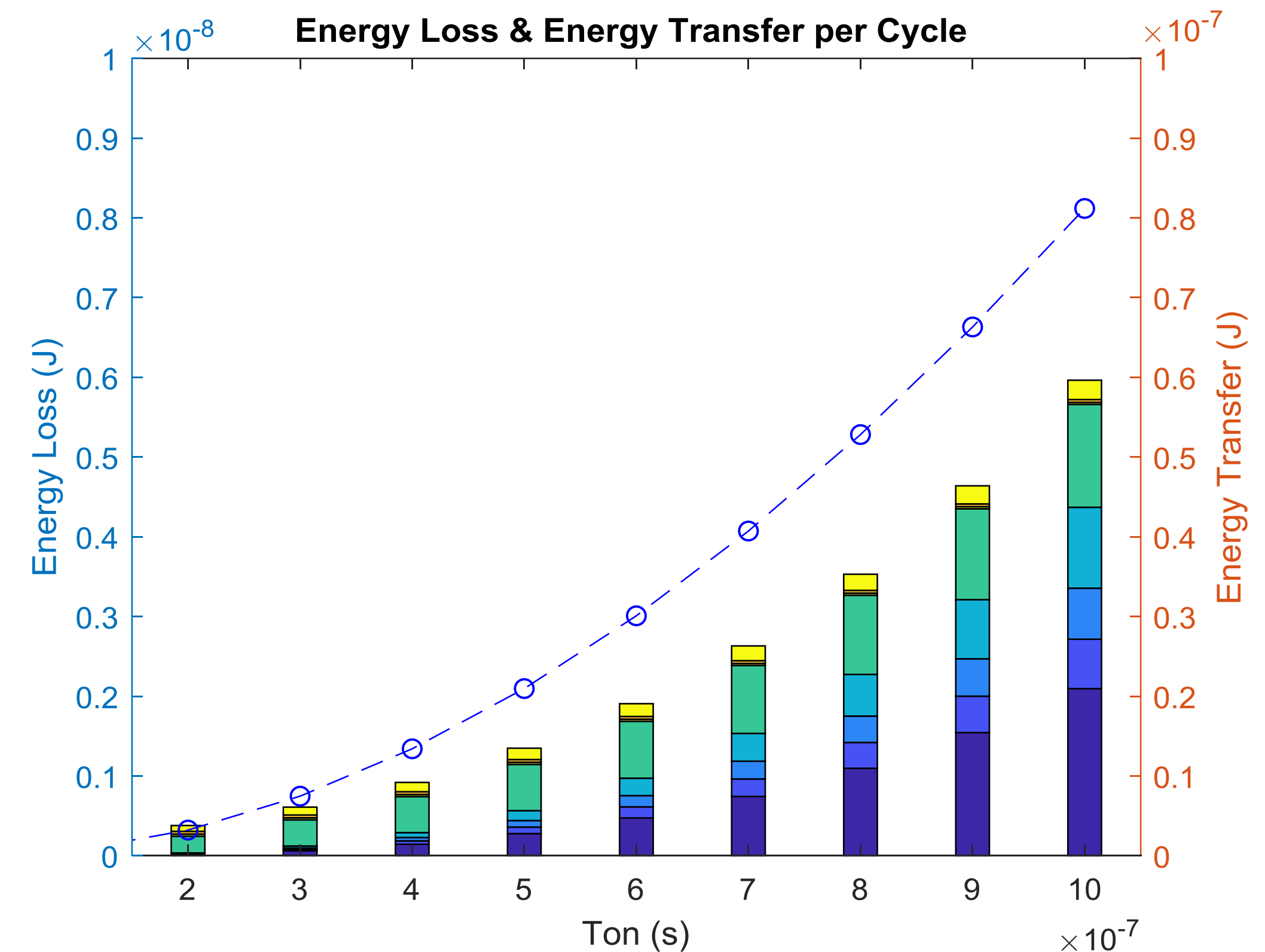
10uW, 1V5-3V3, 22uH Energy Loss and Energy Transfer per cycle vs Ton



Sample IP Blocks



- 4 Switch QR Non Inverting Buck-Boost Power Path for 95% efficiency from 1uW to 10mW
- Mixed signal innovative architecture
- Extra low input voltage operation
- Asynchronous PWM Modes Generation
- Ultra efficient power path, gate drives and level shifters design
- 20nA Voltage Comparator
- 10ns Current Input Comparator
- 10ns High Side Voltage low voltage threshold Comparator
- Starved Inverter Ring Oscillators
- <100nA Cold Start: Oscillator/Charge Pump/Fractional reference system
- SPI Master Configurable Mixed Signal (external Serial EEPROM)
- High speed analog event detect latches (power cycleable)
- Variety of Digital-to-time converters (DTC)
- Ultra Low Energy ADC Systems
- Asynchronous master control state machines
-

80+% efficiency @ 1 μ W

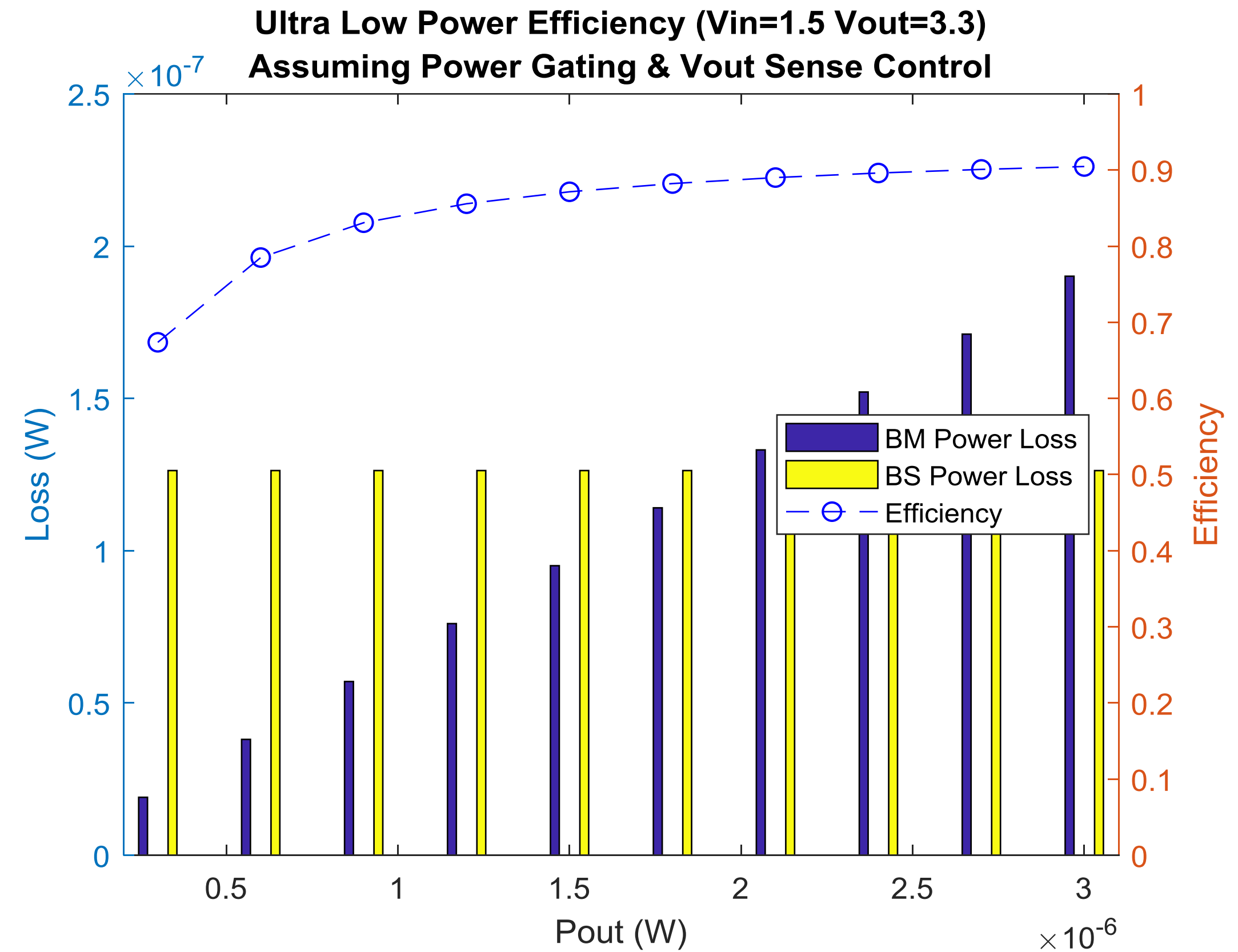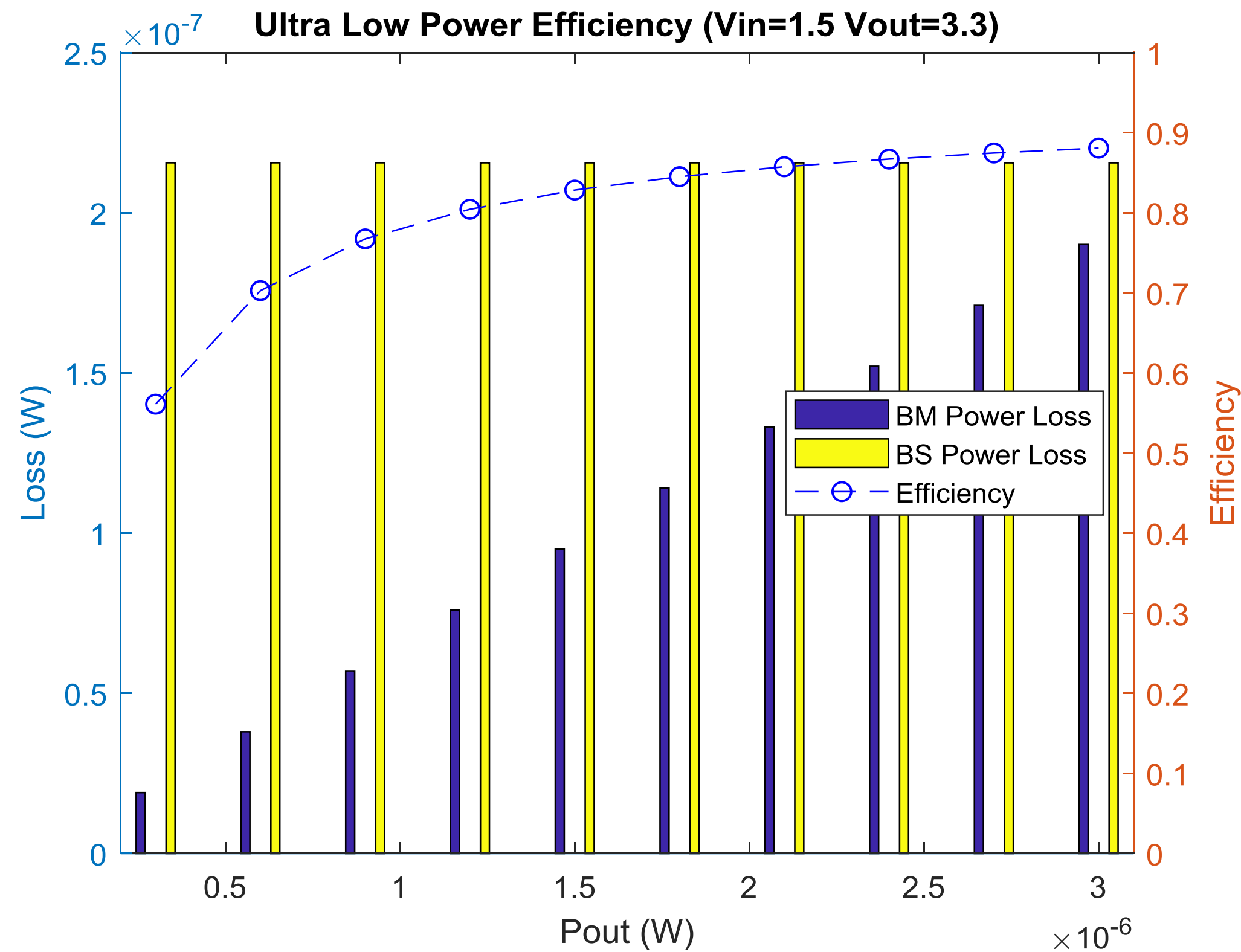

Mischief vs Commercially Available Parts (2017)

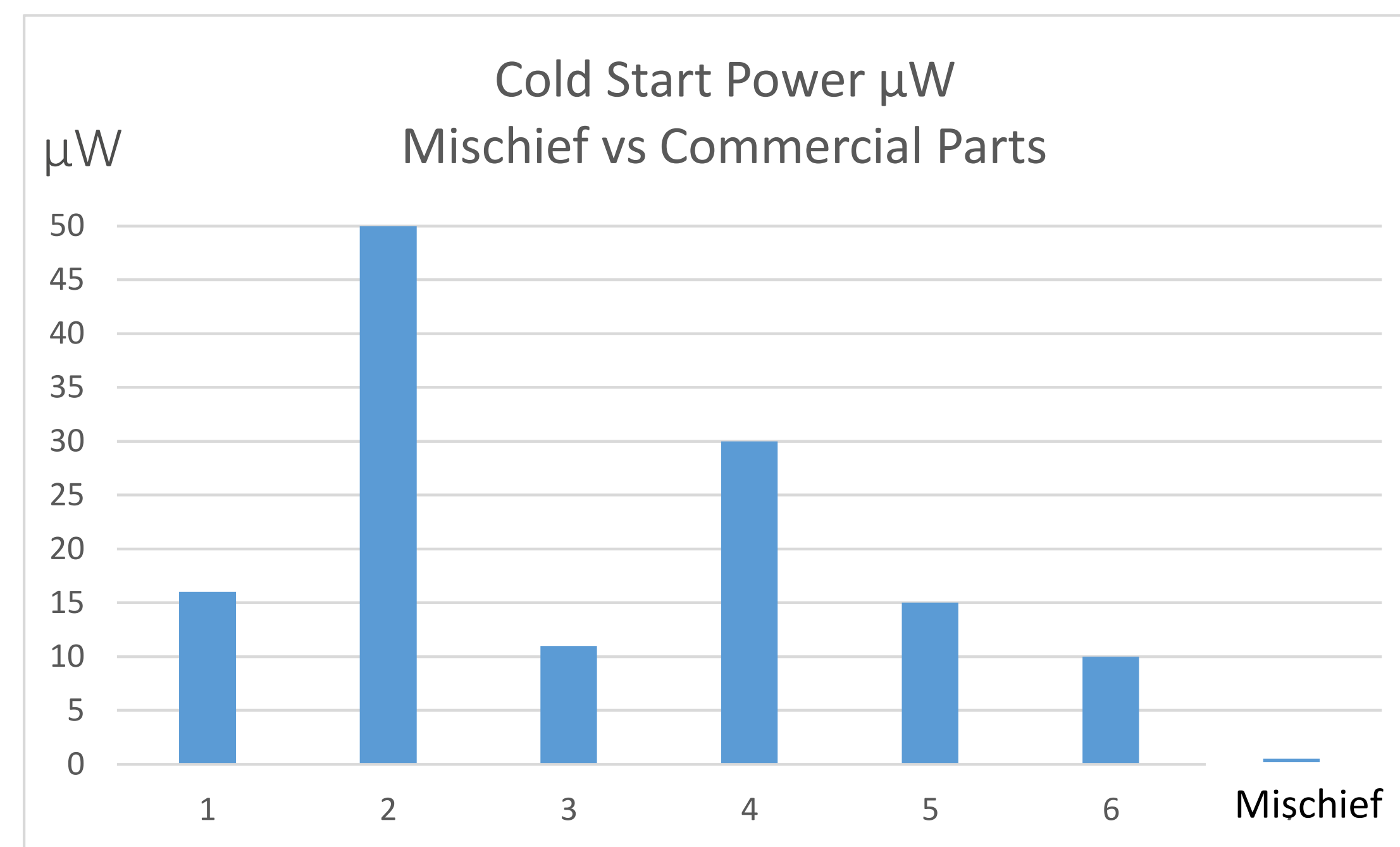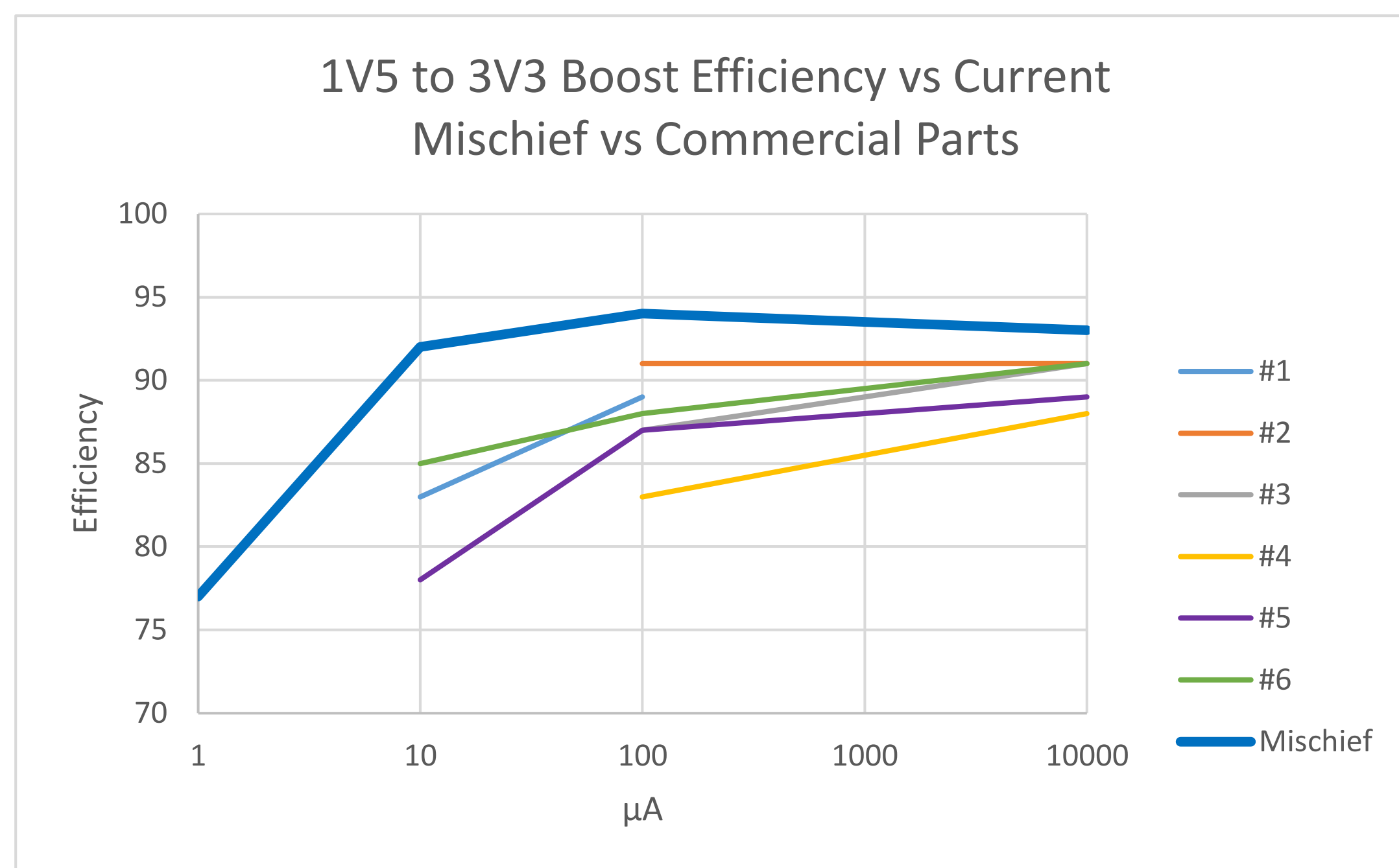Only one part surveyed has buck-boost capability
None have advanced digital configurability (SPI)




Mischief based on Top Level Schematic Sims (not LVS)

Part nos ADP5090, MB39C831, AEM10940, SPV1050, BQ25504, MAX17220

Mischief versus Commercially Available parts

Low V_{IN} operation (after Cold Start)

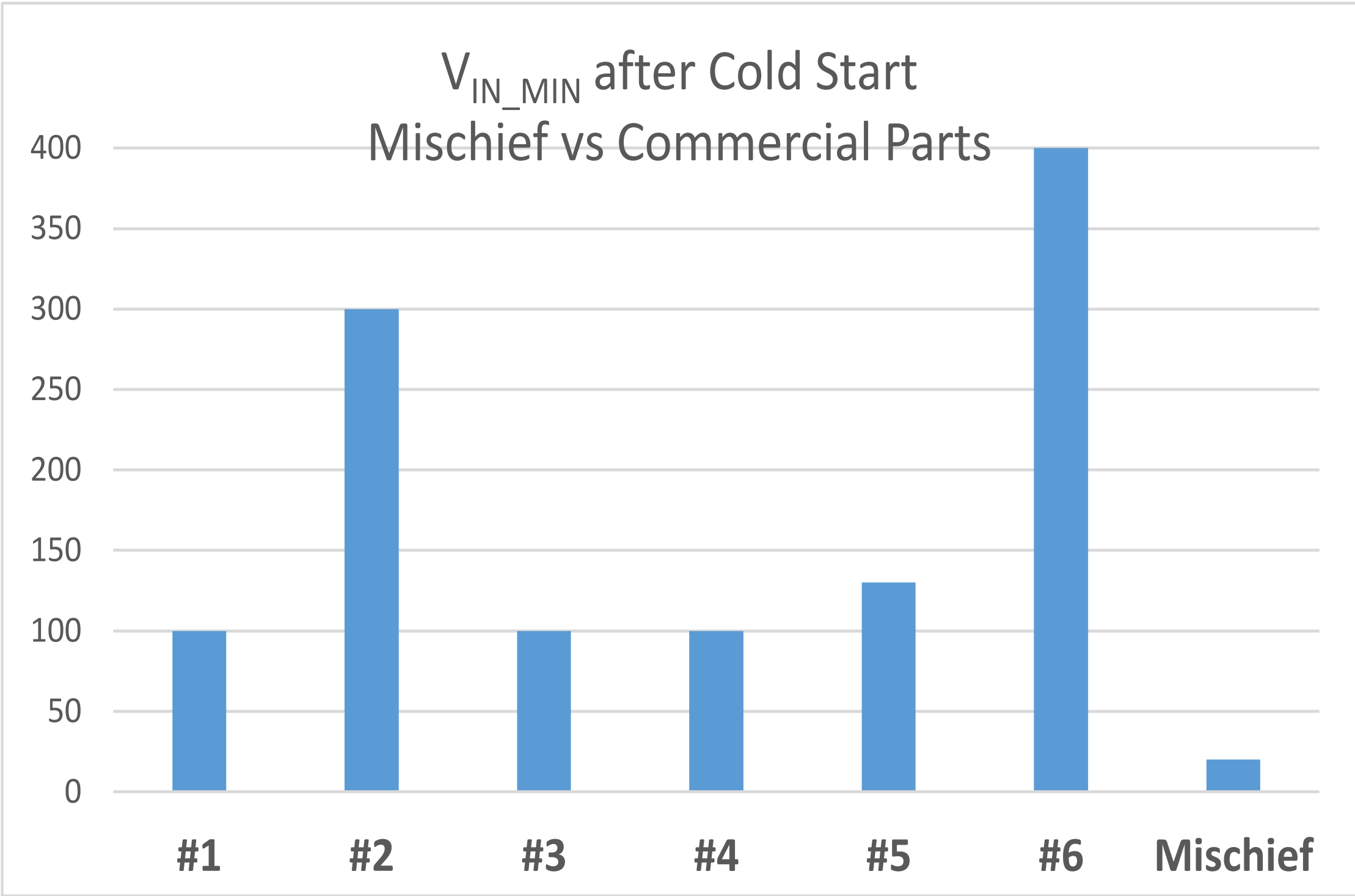


Marketplace EH PMIC	SPI/ I2C Interface with Host WSN Controller	Topology	Low Output Voltages
#1	No	Boost	No
#2	No	Boost	No (3V+)
#3	No	Cascade Boost, Buck+LDO	Yes
#4	No	Boost, Buck-Boost, LDO	Yes
#5	No	Boost	No (2V+)
#6	No	Boost	No
Mischief	Yes	Buck-Boost	Yes (1V+)

Control & Drive Efficiency vs Research

(considering 100 X Po difference between these designs)

IBM, MIT Research ISSCC'17 65nm

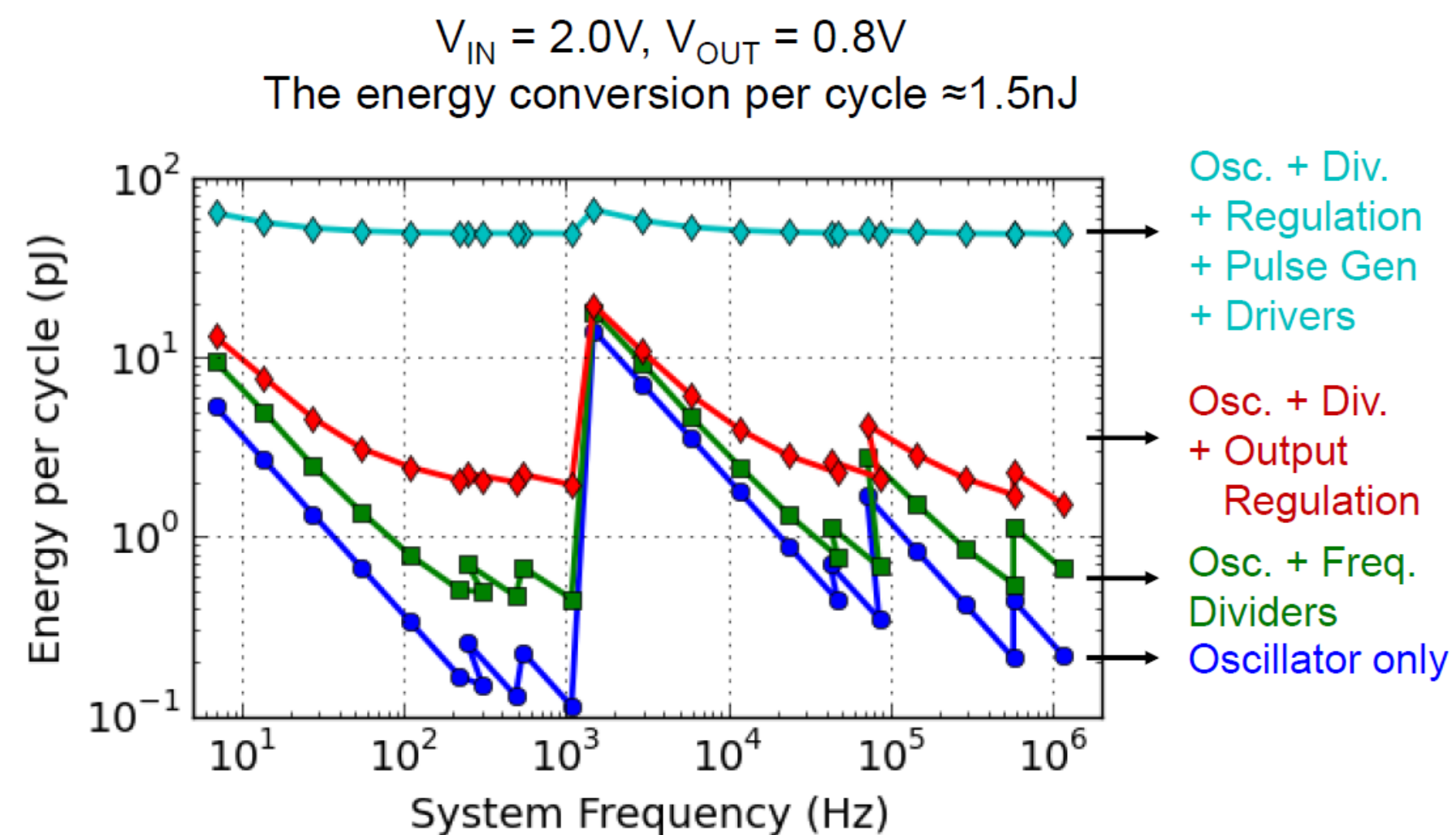Overall Control Energy Loss for 240 pW Quiescent (0.8mW *max*) Buck Converter 2V-0.8V, 47uH (65nm CMOS)




Energy Out \div (Control+Drive) Energy per Cycle \Rightarrow
($\eta_{CONTROL}$) = 95.6%

A Buck Converter with 240pW Quiescent Power, 92% Peak Efficiency and a 2×10^6 Dynamic Range, Arun Paidimarri, Anantha P. Chandrakasan, ISSCC'17

Tyndall MCCI, Mischief '18 180nm

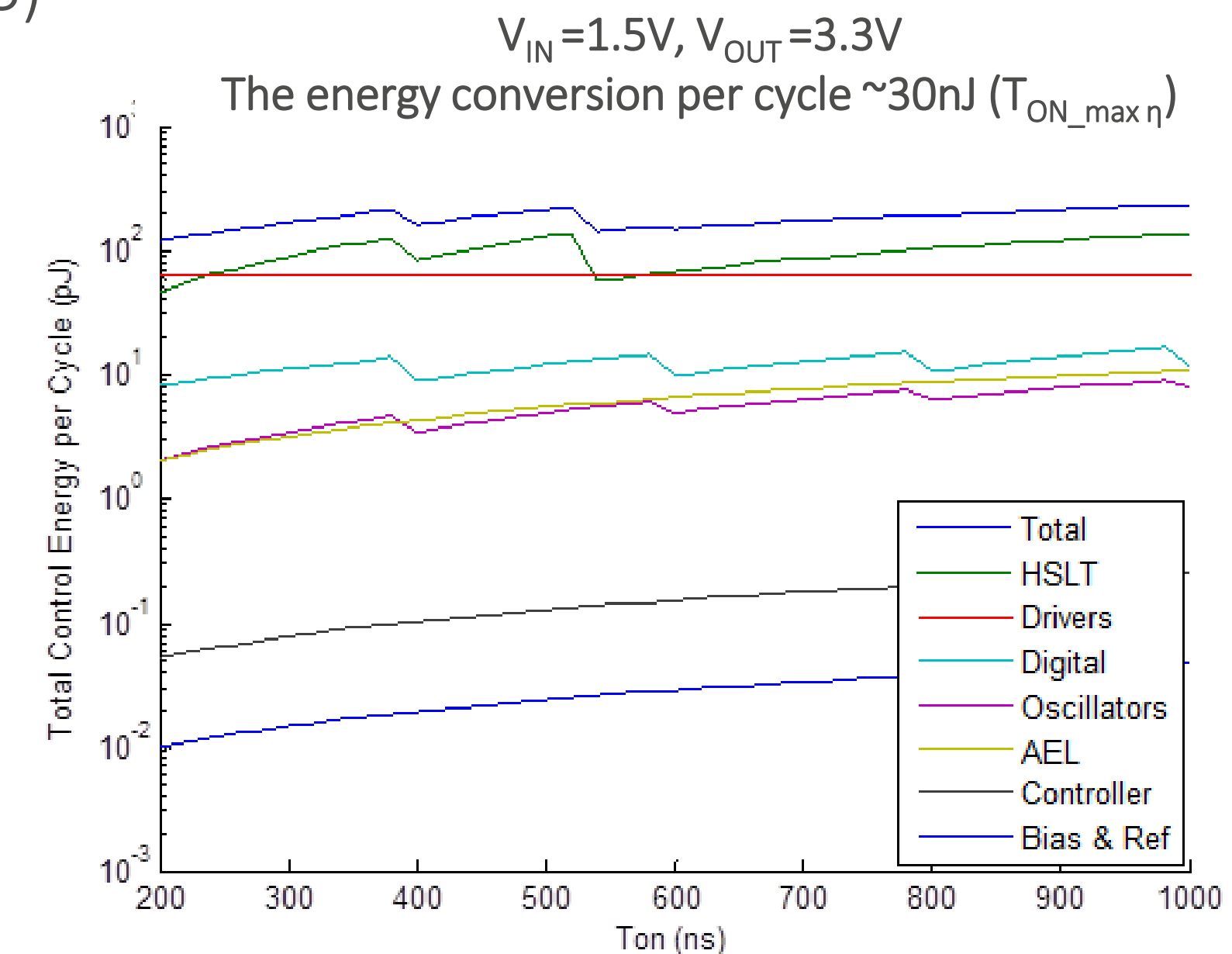Overall Control Energy Loss for 200 nW Quiescent (27mW @ $T_{ON_max \eta}$) Buck-Boost Converter 1V5-3V3, 22uH (180nm CMOS)



Energy Out \div (Control+Drive) Energy per Cycle \Rightarrow
($\eta_{CONTROL}$) = 98.83% (@ $T_{ON_max \eta} = 600ns$ (max. η))

S3_GD = 27pJ, S4_GD = 34pJ @ $T_{on} = 600ns$ for 1V5 to 3V3, 1kHz/1ms Burst Space assumed = 200pJ

Conclusions

Advanced real time system optimisation is feasible for highly featured 350nW+ designs

Advanced digital modulators and control are applicable, next step - add ULE ADC
Digital filtering and outer loops may be implemented by node host controller

Power System Design selects T_{ON} for maximum efficiency at all points – Host -> SPI -> Config Benefit

Extensive Matlab modelling and top level Cadence simulation match-up

Our Control and Modulator Energy Efficiency is very high

Our Quiescent Current could be substantially reduced by HSLT redesign, switched senses and power gating

Our architecture is future proofed for considerably higher frequencies

Our architecture is applicable for maximising energy transduction and efficiency for a wide range of emerging MEMs and Micro Scale Systems

IP for IoT Node ASICs, SoCs

Team

- James McCarthy
- Tim Daly
- Gerry McGlinchey
- Ivan O'Connell, Séamus O'Driscoll

Thank You